

SP ENGINEERING ACADEMY

Video Lectures / Course Materials

COMPLETE COURSE

DIGITAL SYSTEMS

DIGITAL CIRCUIT DESIGN

Lecture Series #09 - Digital Comparators

Topic #	Content	
103	Design of 2 Bit Digital Comparator - Truth Table, Logic Circuit and Explanation - https://youtu.be/YsixHklZI1s	02
104	Design of One Bit Digital Comparator - Truth Table, Logic Circuit and Explanation - https://youtu.be/Glu27lyXI_s	05
105	Design of 4 Bit Digital Comparator - Truth Table, Logic Circuit and Explanation - https://youtu.be/m3HwoWaBV_Q	06
106	4 Bit Comparator IC 7485 - Pin Configuration, Truth Table and Explanation - https://youtu.be/7l2Ki	09

Example 01

Video Link - <https://youtu.be/YsixHklZ1Is>

Design 2-bit Comparator using gates

The truth table for 2-bit Comparator is

Inputs				$A > B$	Outputs	
A_1	A_0	B_1	B_0		$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

$A_1 A_0$	$B_1 B_0$				$A > B$
	00	01	11	10	
00					
01	1				
11	1	1		1	
10	1	1			

$$A > B = A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{B}_1 + A_1 A_0 \bar{B}_0$$

A, A_0 B, B_0 $A = B$

	00	01	11	10
00	1			
01		1		
11			1	
10				1

A, A_0 B, B_0 $A < B$

	00	01	11	10
00		1	1	1
01			1	1
11				
10			1	

$$(A = B)$$

$$= \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0$$


$$+ A_1 A_0 B_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0$$

$$= \bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) + A_1 B_1 (A_0 B_0 + \bar{A}_0 \bar{B}_0)$$

$$= (A_0 \odot B_0) (A_1 \odot B_1)$$

$$(A < B) = \bar{A}_1 \bar{A}_0 \bar{B}_0 + \bar{A}_0 B_1 B_0 + \bar{A}_1 B_1$$

A_1 A_0 B_1 B_0

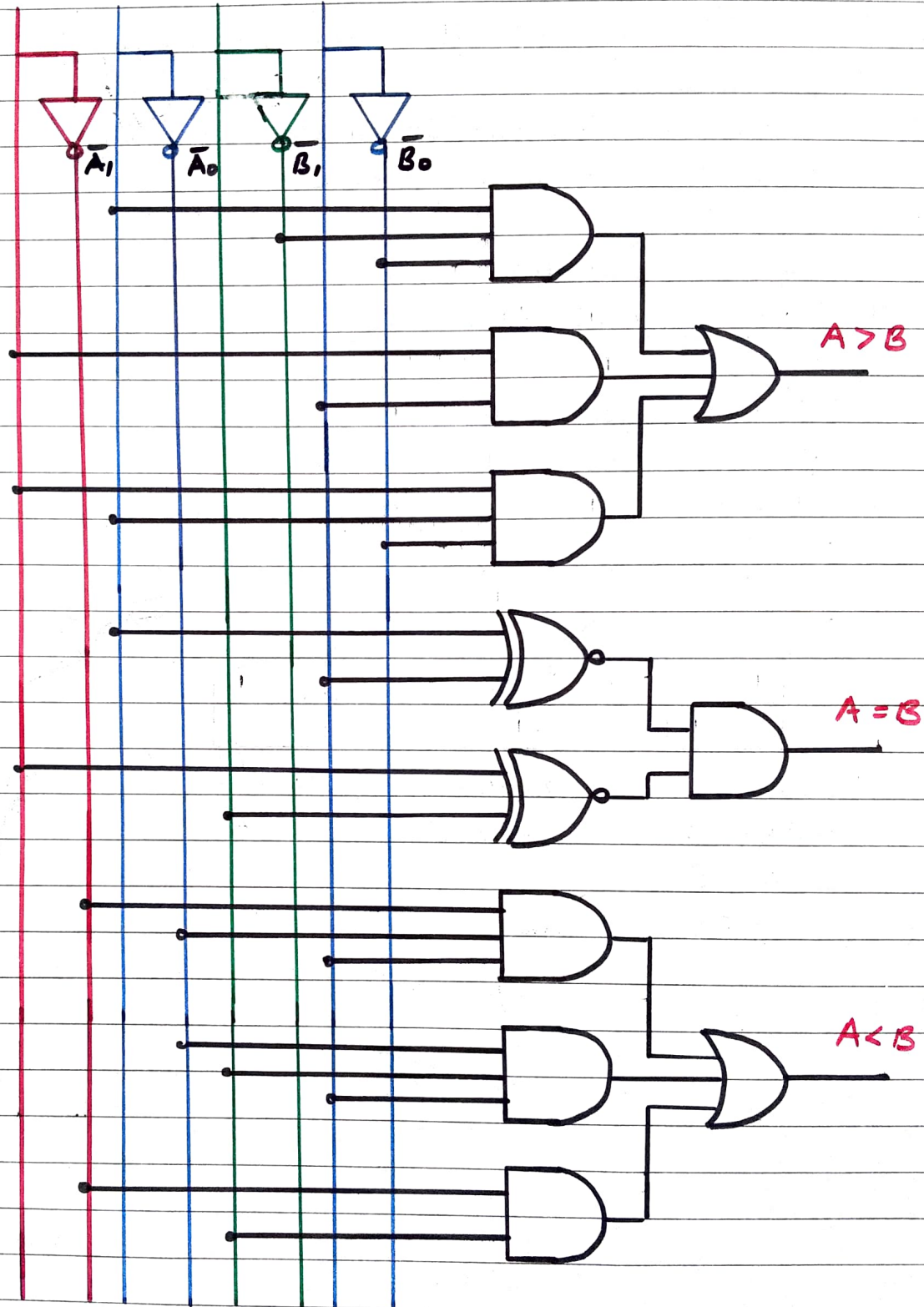

Example 02


Video Link - https://youtu.be/Glu27lyXI_s

Design a 1 bit Comparator using logic gates

Consider a two one bit number A and B.

The truth table is shown below


Inputs		Output Y		
A	B	A=B	A>B	A<B
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

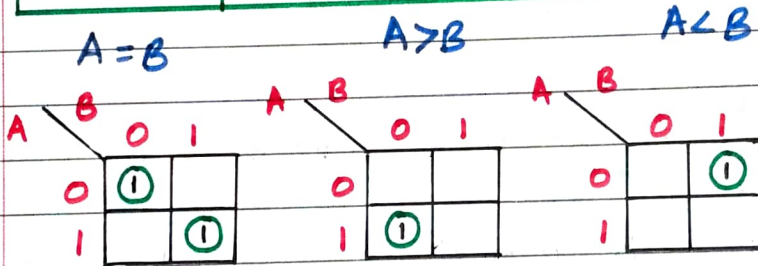

$$\begin{aligned}
 Y_{A=B} &= \bar{A}\bar{B} + AB \\
 &= \overline{A \oplus B} \\
 &= A \odot B
 \end{aligned}$$

$$Y_{A>B} = A\bar{B}$$

$$Y_{A<B} = \bar{A}B$$

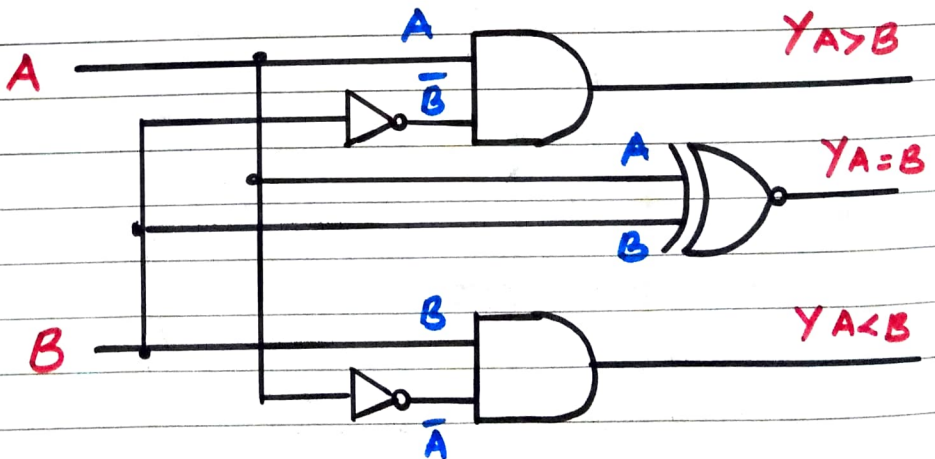

Example 03

Design a 4-bit magnitude Comparator

Comparison Algorithm

$$A = B$$

→ Consider two 4-bit binary numbers A and B such that

$$A = A_3 A_2 A_1 A_0 \quad \text{and} \quad B = B_3 B_2 B_1 B_0$$

→ Two numbers are said to be equal when $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = B_0$

→ In binary, the equality of each pair of bits can be expressed logically with an exclusive NOR function as

$$x_i = A_i B_i + \bar{A}_i \bar{B}_i \quad \text{for } i=0,1,2,3$$

where $x_i = 1$ only if the pair of bits in position i are equal (i.e. both are 1 or 0)

→ Therefore we can say that

$$A = B, \quad \text{if } x_0 \cdot x_1 \cdot x_2 \cdot x_3 = 1$$

$$(A > B) \text{ or } (A < B)$$

→ To determine whether A is greater or less than B, it is necessary to inspect the relative magnitudes of pairs of significant digits, starting from the most significant position

→ If the two digits of a pair are equal, we compare the next lower significant pair of digits. The comparison continues until a pair of unequal digits is reached

→ If Corresponding digits of A is 1 and that of B is 0, we say that $A > B$

→ If Corresponding digits of A is 0 and that of B is 1, we say that $A < B$


→ The sequential expression to determine whether $A > B$ or $A < B$ are as given below

$$(A > B) = A_3 \bar{B}_3 + x_3 A_2 \bar{B}_2 + x_3 x_2 A_1 \bar{B}_1 + x_3 x_2 x_1 A_0 \bar{B}_0$$


$$(A < B) = \bar{A}_3 B_3 + x_3 \bar{A}_2 B_2 + x_3 x_2 \bar{A}_1 B_1 + x_3 x_2 x_1 \bar{A}_0 B_0$$

The block diagram of an n-bit Comparator is shown below. It receives two n-bit numbers A and B as inputs and the outputs are $A > B$, $A = B$ and $A < B$.

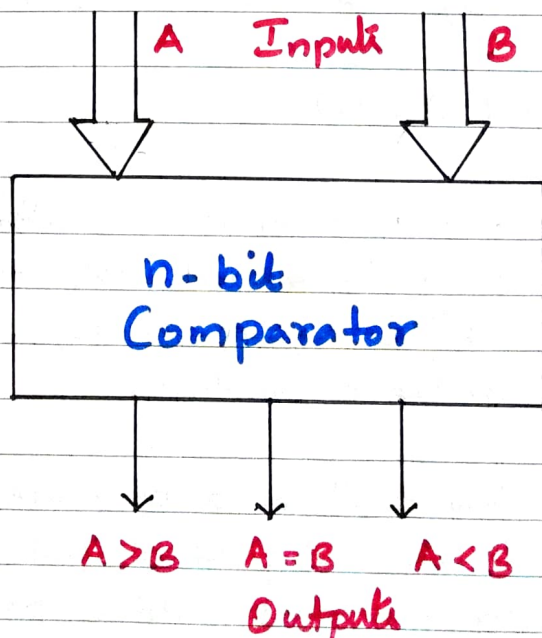
Depending upon the relative magnitudes of the two number, one of the outputs will be high.




Ex-NOR

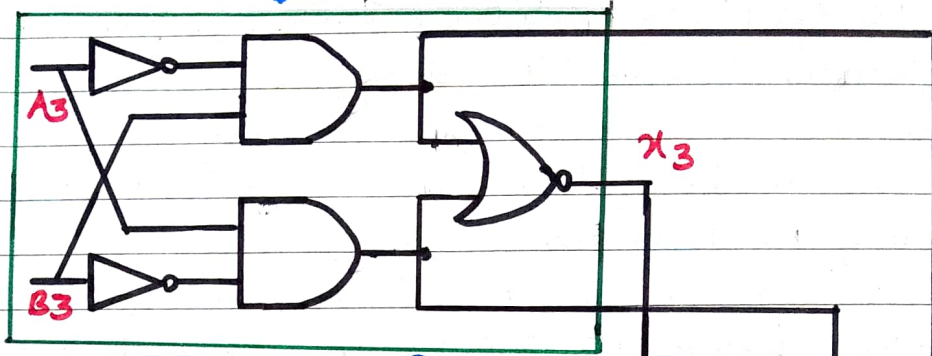



Ex NOR

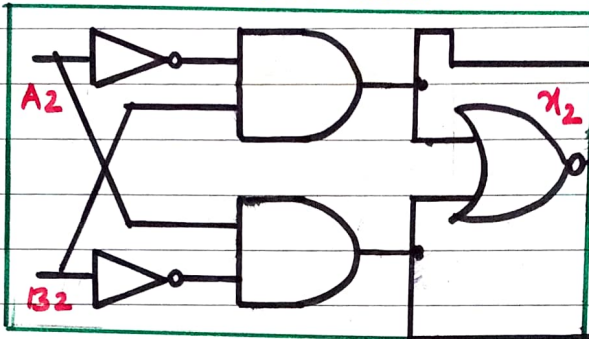

Ex NOR

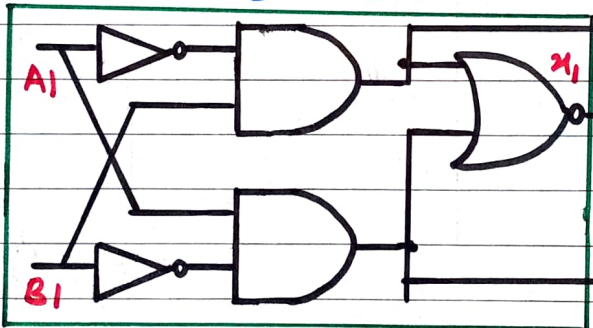

Ex NOR

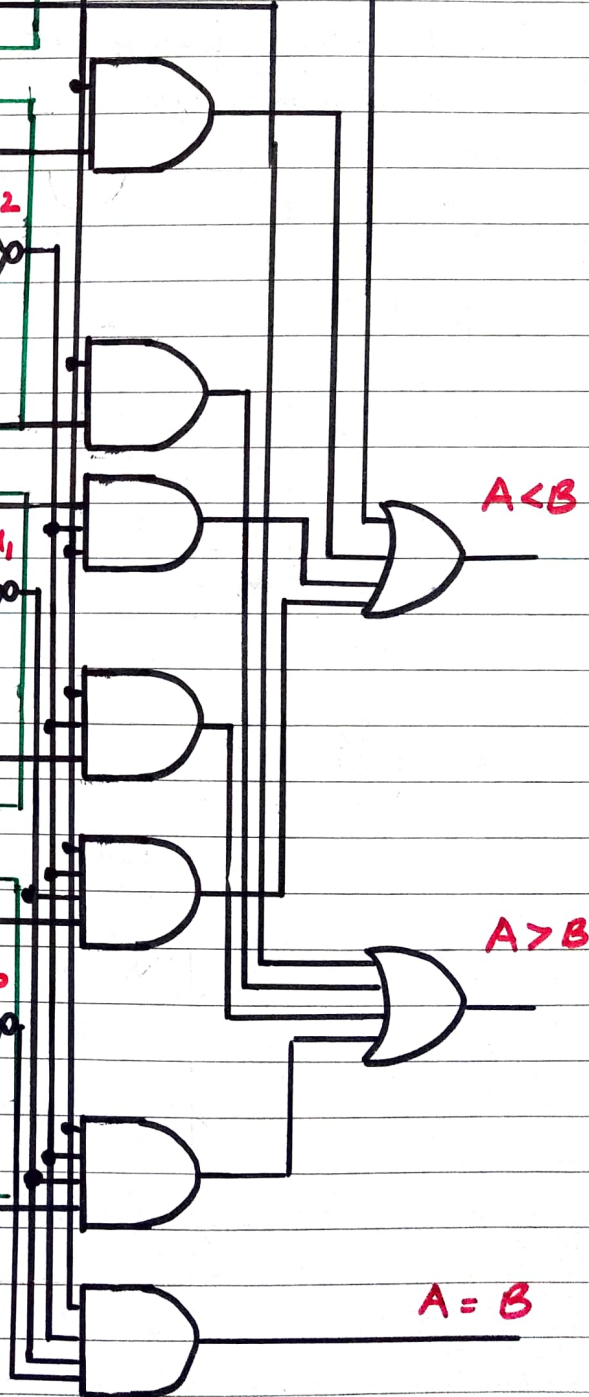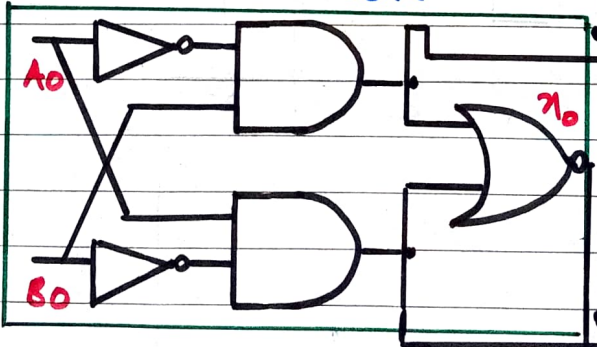

IC 7485 is a 4-bit Comparator. It can be used to Compare two 4-bit binary words by grounding $I(A < B)$, and $I(A > B)$ and Connecting input $I(A = B)$ to V_{CC} . These IC's can be Cascaded to Compare words of almost any digits lengths. Its 4-bit inputs are weighted ($A_0 - A_3$) and ($B_0 - B_3$), where A_3 and B_3 are the most significant bits

B_3	1	16	V_{CC}
$I(A < B)$	2	15	A_3
$I(A = B)$	3	14	B_2
$I(A > B)$	4	13	A_2
$A > B$	5	12	A_1
$A = B$	6	11	B_1
$A < B$	7	10	A_0
GND	8	9	B_0

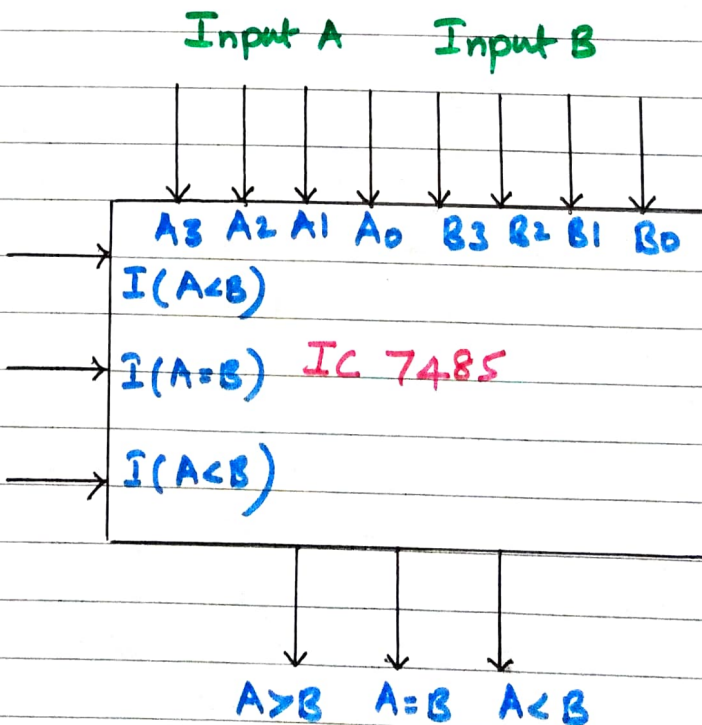


Diagram shows the logic symbol and pin diagram of IC 7485.

The operation of IC 7485 is described in the function table, showing all possible logic conditions.

Comparing Inputs A B	Cascading Inputs			Outputs		
	$I(A > B)$	$I(A = B)$	$I(A < B)$	A > B	A = B	A < B
A > B	x	x	x	1	0	0
A = B	1	0	0	1	0	0
	x	1	x	0	1	0
	0	0	1	0	0	1
	0	0	0	1	0	1
	1	0	1	0	0	0
A < B	x	x	x	0	0	1