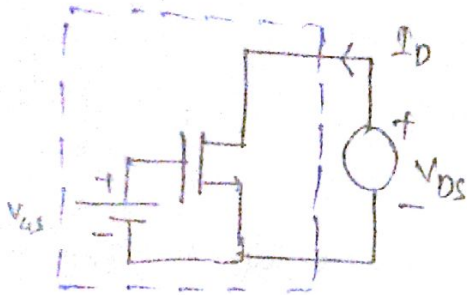


Lecture - 31

* I-V characteristics (continued) *

If $V_{DS} \ll 2(V_{GS} - V_{th})$ then


$$I_D \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) V_{DS}$$



* V_{DS} is small

$$I = \frac{V}{R}$$
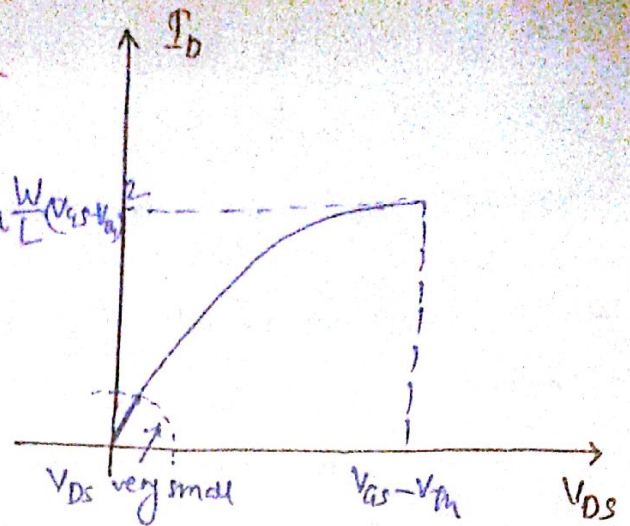
$$R_{ON} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})}$$



→ This says that MOS device can work as a resistor, when V_{DS} is not too large. Since this resistance value is in our control so it is called as electronically adjustable resistor / electronically tunable resistor.

→ A MOSFET can act as a voltage dependent resistor (if $V_{DS} \ll V_{GS} - V_{th}$).

* MOS device as a switch:-




→ If the Gate voltage is high enough then we have a finite resistance between source to drain.

→ If the Gate voltage is low enough then device turns off, we have infinite resistance. So it's like a switch but it's not a ideal switch because it has some resistance when it is ON.

at once the V_{DS} reaches $V_{GS} - V_{TH}$ and increases then the I_D becomes constant.

* I_D for $V_{DS} > V_{GS} - V_{TH}$

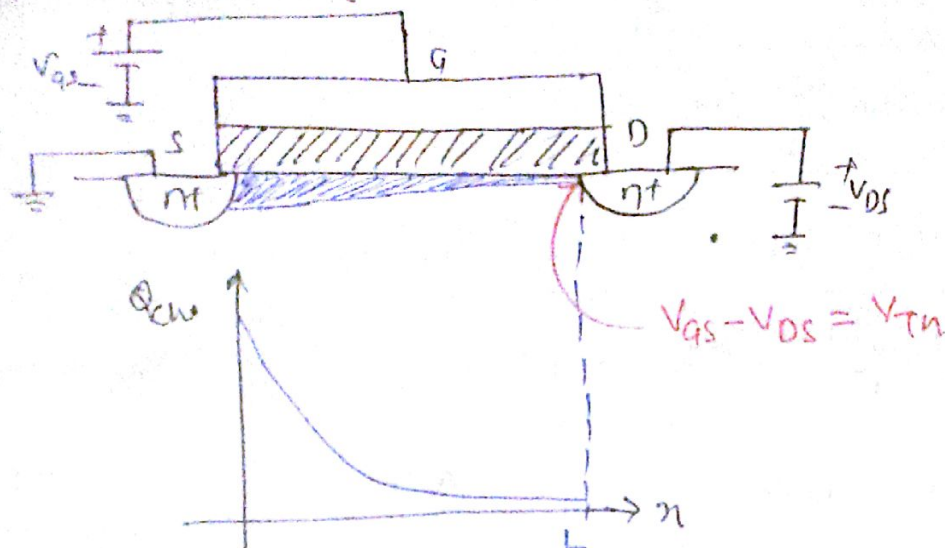


→ The charge density may fall to zero if the voltage difference at drain is not enough to create free electrons at the edge of channel.

⚡ If at the edge $V_{GS} - V_{DS} = V_{TH}$ then there is no charge density.

If $V_{GS} - V_{TH} > V_{DS}$ then there is some charge.

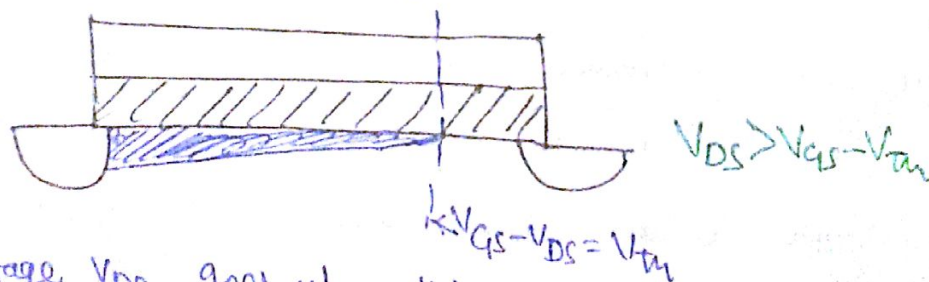→ If V_{DS} goes beyond $V_{GS} - V_{TH}$ then point at which the charge density goes to zero is no longer here it's a little further back. The point at which charge density became zero is called pinch off.



→ As the voltage V_{DS} goes up, this point moves to the left very slowly, it's a very weak function. The total channel length does not change much.

Derive the I_D/V eqn:-

$$\int_0^L I_D dx = \mu_n C_{ox} \frac{W}{L} \int_0^{V_{GS} - V_{TH}} (V_{GS} - V_{TH} - V(x)) dV$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$


for $V_{DS} \geq V_{GS} - V_{TH}$
Saturation Region

This is equation beyond the pinch off.

$$I_D = \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2}]$$


Triode (Linear) region
 $V_{DS} \leq V_{GS} - V_{TH}$

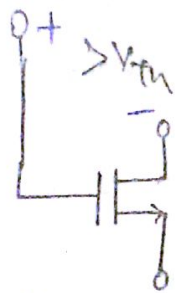→ If the Gate voltage is low enough i.e. $V_{GS} < V_{TH}$ then device is off, i.e., cutoff.



$$V_{DS} < V_{GS} - V_{TH}$$

Triode (Linear) region

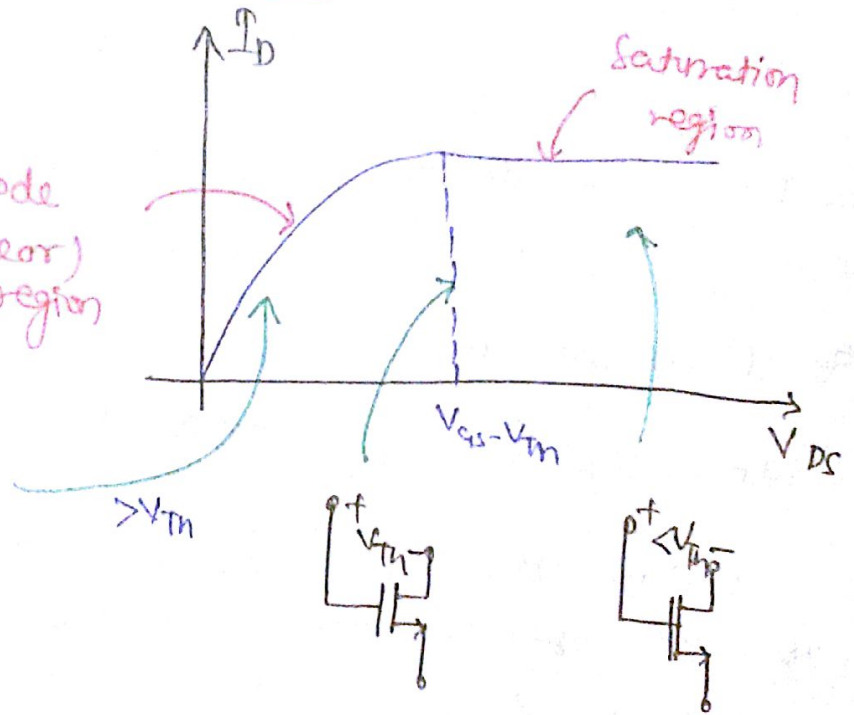


→ If the gate is above the drain by more than one threshold V_{TH} then we are in triode region.

→ If the gate and drain have potential difference V_{TH} then it is at edge.

→ If the gate is below the drain by ^{more} V_{TH} then we are in saturation region.

Observation:-

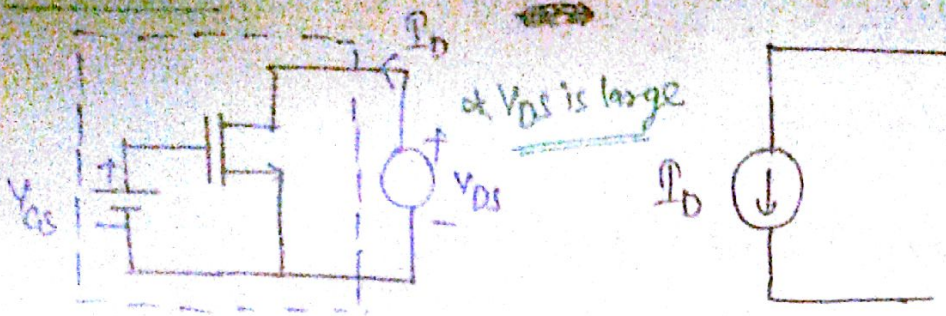


→ If V_{DS} is varying by large amount then current does not vary i.e. current is constant in device so it works as current source.

at I_D v/s V_{GS} characteristics:-

→ If V_{GS} is below V_{TH} , device is off.

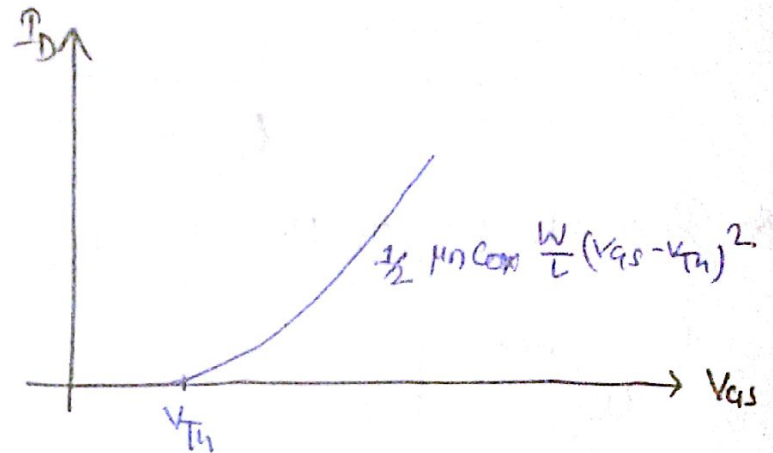→ If V_{GS} exceeds V_{TH} , we use saturation equation which has square law behaviour.



Exercise:- Prove that the MOS device always ON in saturation if $V_{DS} > 0$.


Since MOS device becomes ON,

$$V_{GS} > V_{TH}$$

$$\text{So } V_{GS} - V_{TH} > 0$$


$$\text{that means } V_{DS} \geq V_{GS} - V_{TH}$$

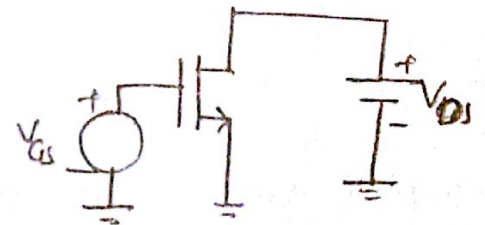This condition occurs in saturation. Therefore MOS device always ON in saturation if $V_{DS} > 0$.



* Simple Model:- In saturation,

voltage dependent current source

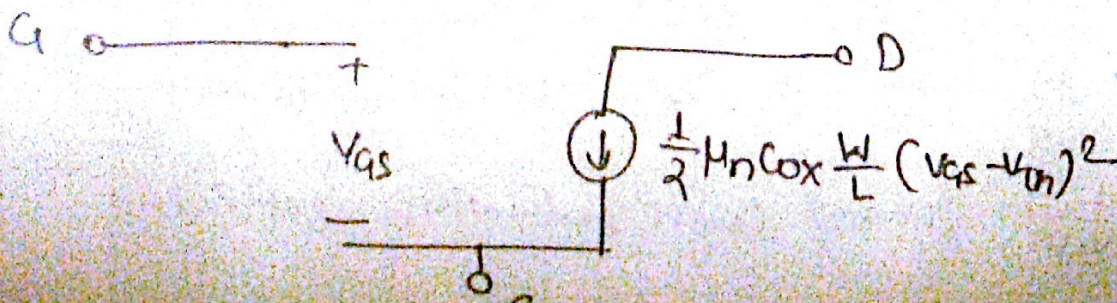

Example:


$$\mu_n C_{ox} = 100 \mu A/V^2, V_{th} = 0.5V, \frac{W}{L} = \frac{5 \mu m}{0.5 \mu m}$$

Design a 1mA current source.

$$1mA = \frac{1}{2} \times 100 \times 10^{-6} \times 10 \times (V_{GS} - 0.5)^2$$

$$2 = (V_{GS} - 0.5)^2$$



$$V_{GS} = 1.9V$$

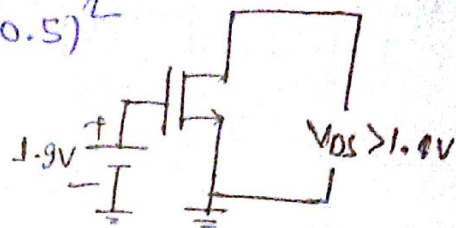

* To act as current source $V_{DS} > 1.4V$.

Lecture - 32

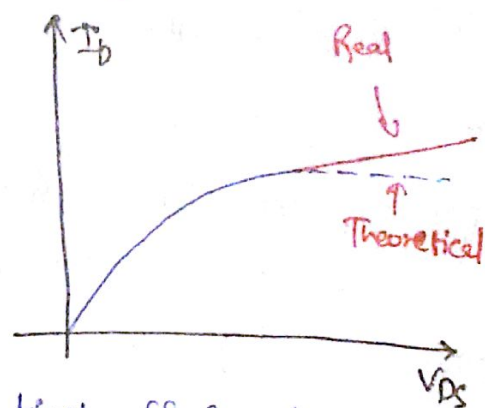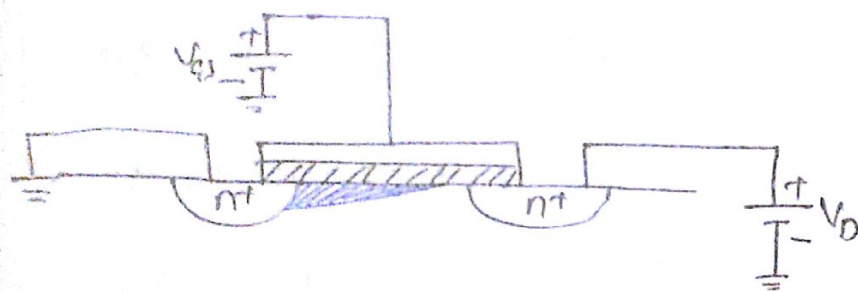* Channel Length Modulation (Similar as Early Effect):-



* Suppose we are in saturation so we have pinch off in channel.


→ As $V_{DS} \uparrow$, the channel length L decreases by small amount. Since L is inversely proportional to I_D . That means I_D depends on V_{DS} also in saturation.

$$I_D = \frac{1}{2} C_{ox} \mu_n \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda \cdot V_{DS})$$


This tells us that as V_{DS} increases, I_D increases.

$\lambda: \frac{1}{V_{eff}}$ Channel length modulation coefficient


Complete model of MOS Transistor

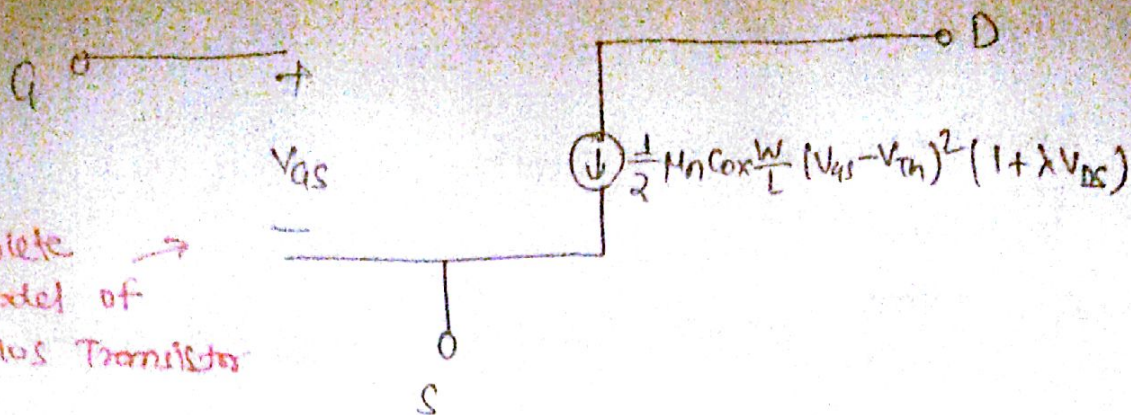

Let's build an amplifier:-

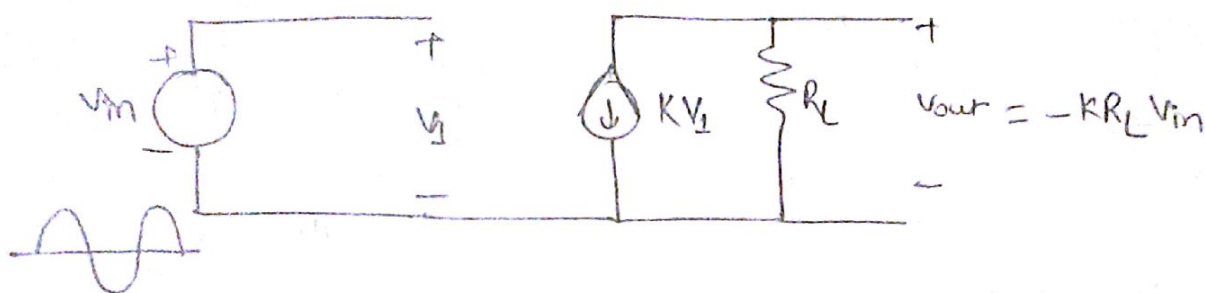



First attempt

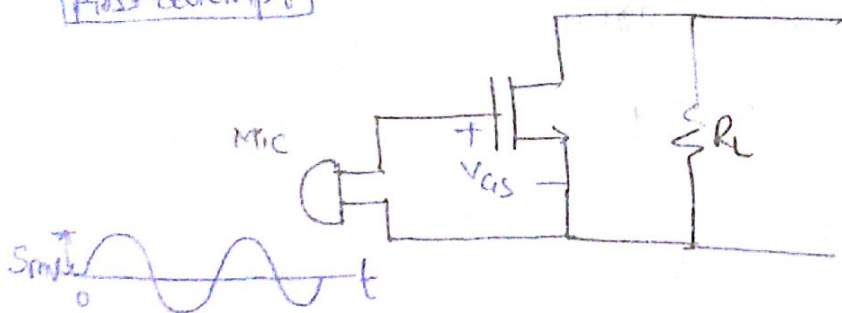

Since device is off until $V_{gs} \geq V_{th}$

Since input signal is so small so $V_{gs} < V_{th}$ therefore device will never turn on.

Second attempt

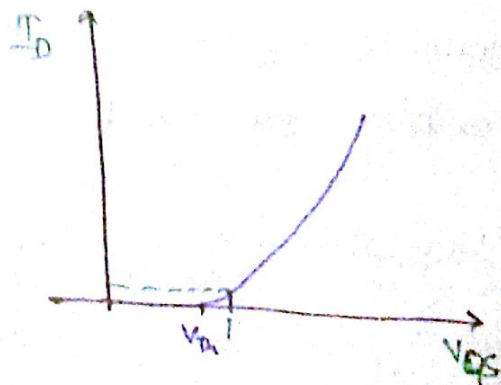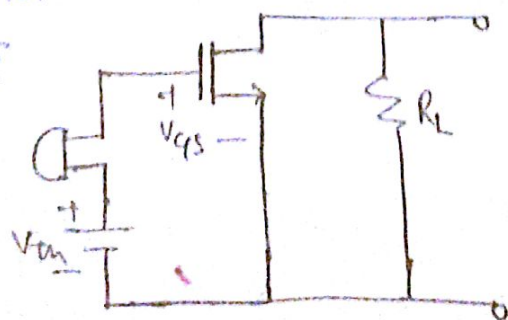

→ If microphone has no signal that means $V_{gs} = V_{th}$. As the signal comes in $V_{gs} - V_{th} = 5\text{mV}$ so we have some current.



$$\mu_n C_{ox} = 100 \mu A/V^2, \frac{W}{L} = 10, V_{Th} = 0.5V$$

$$I_D = \frac{1}{2} \times 100 \times 10^{-6} \times 10 \times (5mV)^2 = 12.5 nAmp.$$

which is so small.

$$R_L = \frac{50mV}{12.5nA} = 4M\Omega \text{ which is very large resistor}$$

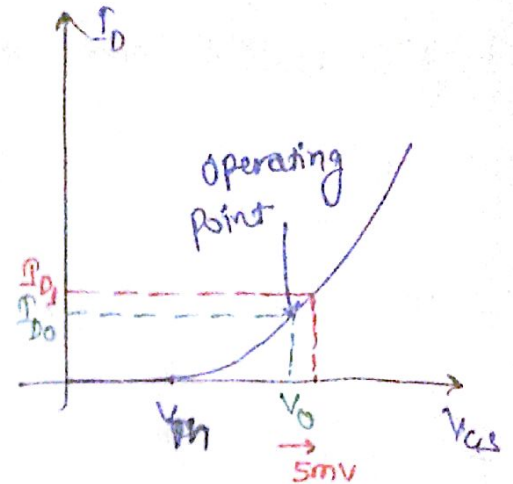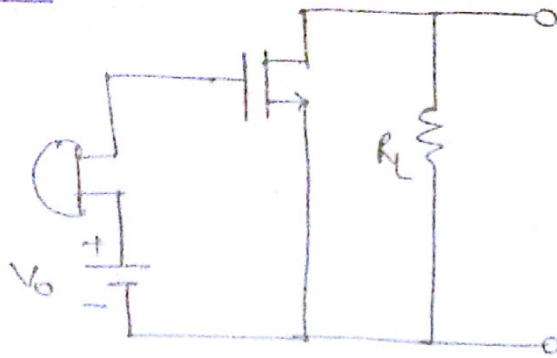Now we move operating point,
Trusted Attempt



$V_0 = 0.9V, V_{Th} = 0.5V$, When no signal

$$I_{D0} = \frac{1}{2} \times \mu_n C_{ox} \frac{W}{L} (0.9 - 0.5)^2 \approx 80 \mu A$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.95 - 0.5)^2 \approx 82 \mu A$$


$$\text{Change in } I_D = 2 \mu A \Rightarrow R_L = \frac{50mV}{2 \mu A} = 25K\Omega$$

* Need to bias the transistor by creating proper current and terminal voltages (in the absence of signal) so that device can amplify the signal.

Observation:- ① A MOS device converts a voltage to a current

$$\text{MOSFET Symbol} \equiv V/I \text{ converter} \Rightarrow \text{Transconductor}$$


② Which operating point is preferred?

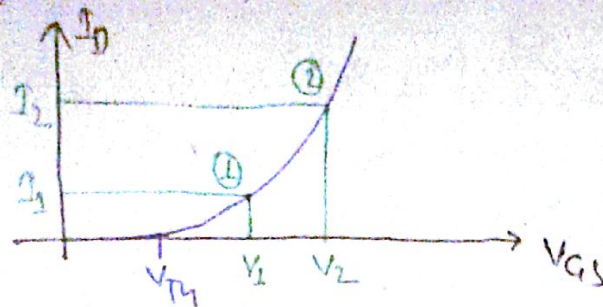

→ For a given input signal change, we get a larger current change at ② than ①. Transistor is better V_{GS} converter at ② than ①. So Point ② will be preferable.


→ When there is no signal, the bias current is draining the battery. If we want more stronger device, so the drain current drains the battery more quickly.

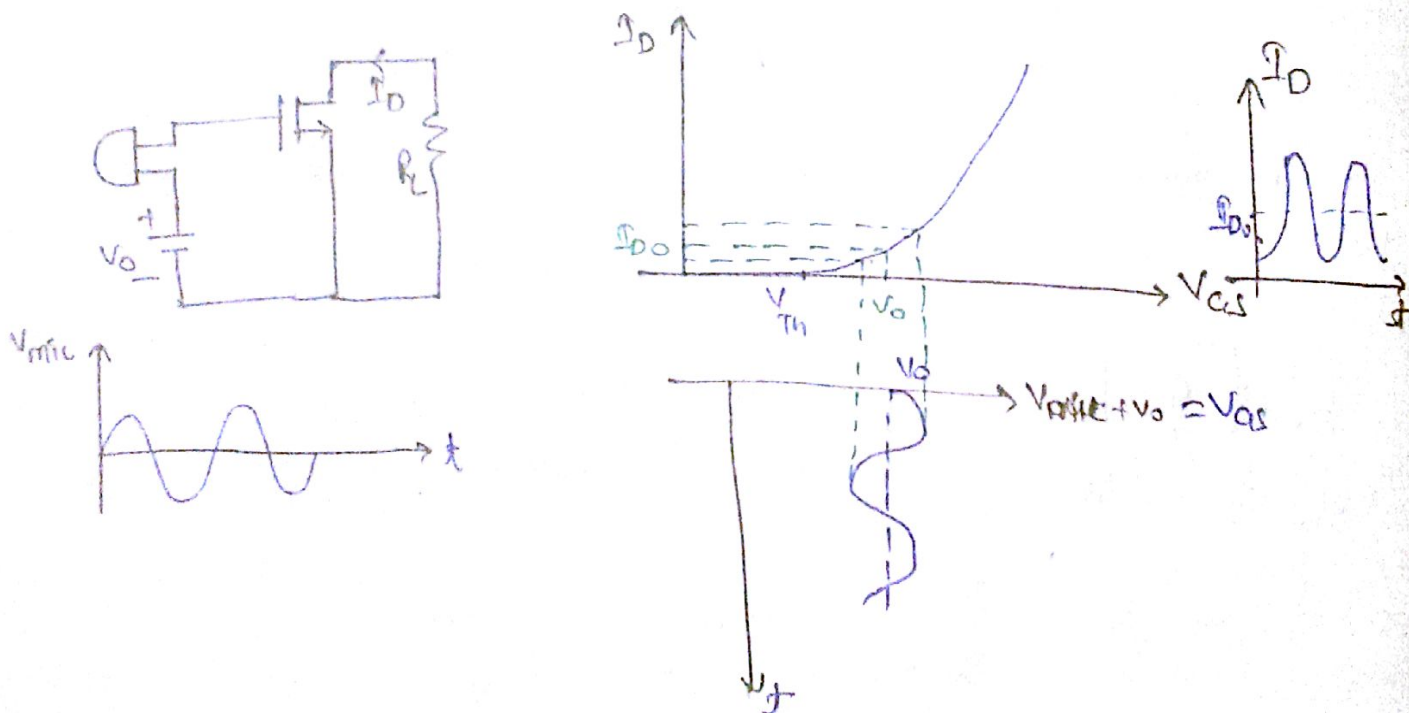* Combining Time response with I/V characteristics:-



Concept of Transconductance:-
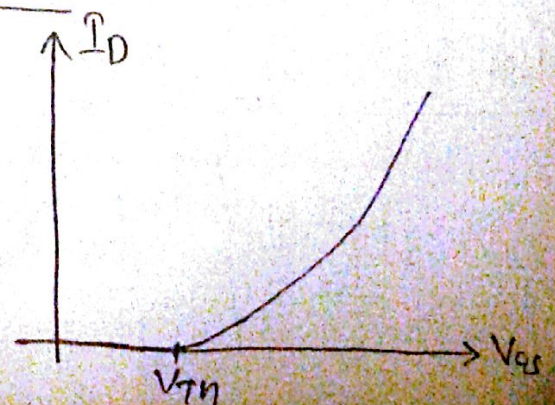
$$g_m = \frac{dI_D}{dV_{GS}} \quad \frac{1}{\Omega} \text{ or Siemens (S)}$$




→ The g_m tells us that how stronger is transistor.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2, \lambda = 0$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$



$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$
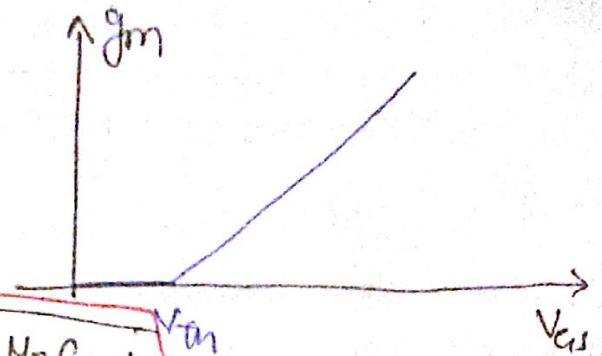
$$g_m = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}}$$



Lecture - 33


Example:-

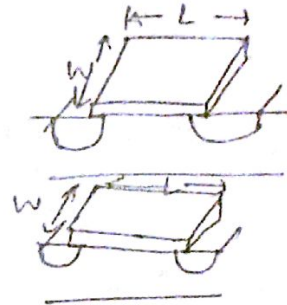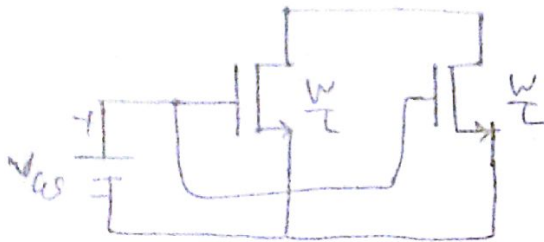

When another mos is connected in parallel with a mos then the combination have $\frac{2W}{L}$.

$$I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$
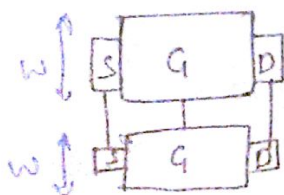
$$I_{D1} + I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{2W}{L}\right) (V_{GS} - V_{TH})^2$$



Since both has same V_{GS} & V_{TH} , μ_n, C_{ox} .

$$\Rightarrow g_m = \frac{2I_{D1}}{V_{GS} - V_{TH}} \Rightarrow \text{New } g_m = 2 \cdot \frac{2I_{D1}}{V_{GS} - V_{TH}}$$

Let build an amplifier:-



* We do need to make sure device is in saturation.


$$V_{DS} > V_{GS} - V_{TH}$$

Ans $V_0 = 0.9V$, $V_{TH} = 0.5V$

for device in saturation,


$$V_{DS} \geq (0.9 - 0.5) \Rightarrow V_{DS} \geq 0.4V$$

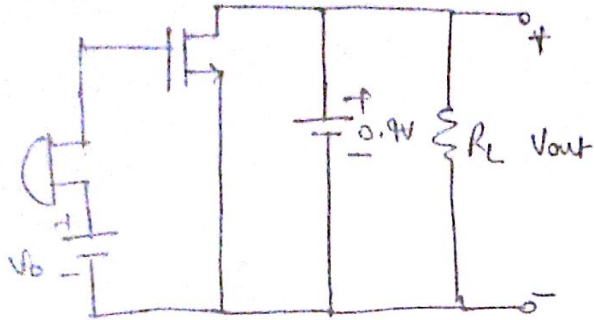Since a dc current can not flow through circuit until it is applied with a source. Therefore V_{ps} would be zero.



Is this device in saturation?

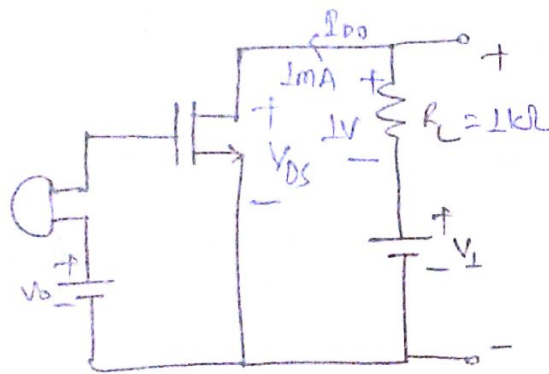Yes, it will be in saturation but we don't have V_{out} we have just 0.4 across the R_L so we don't have output voltage varying time.



$$V_1 = V_{DS} + I_{DQ} R_L$$


$$\Rightarrow V_{DS} = V_1 - \underbrace{I_D R_L}$$

$$0.4 = V_{1-1} \text{ IV}$$

$$\Rightarrow V_1 = 1.9 \text{ V}$$

So for device in saturation we should choose $V_1 = 1.4V$.

* Large signal operation:-

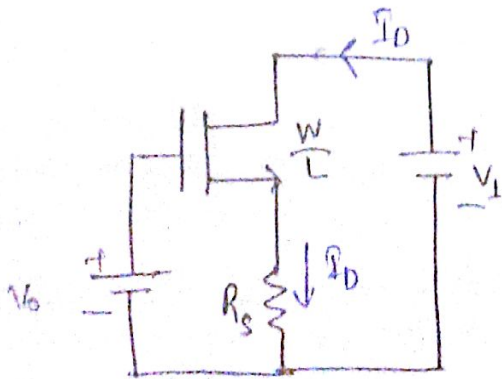


$$V_o = V_{C1s} + I_D R_S$$


$$\therefore V_{gs} = \sqrt{\frac{2 I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{th}$$

$$\textcircled{2} \quad V_0 = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TN} + I_D R_S$$

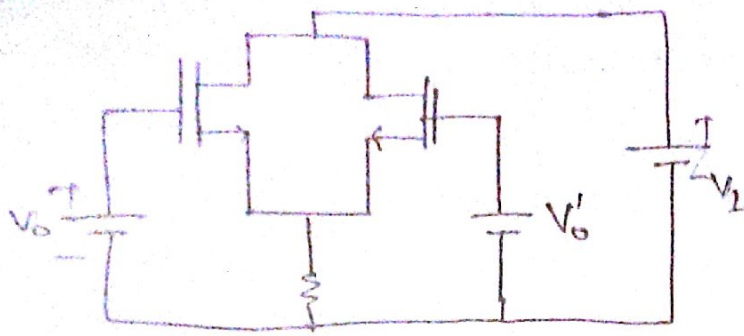Previous results would not help if we have another types of ckt,




Let's add a signal :-

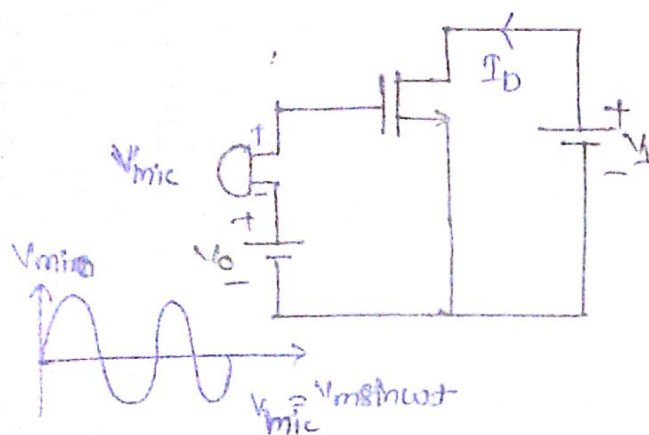


$$V_0 + V_m \sin \omega t = \sqrt{\frac{2 I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{th} + I_D R_s$$

This is called large signal operation, if V_m is not small.

⇒ Use large signal model of Transistor:

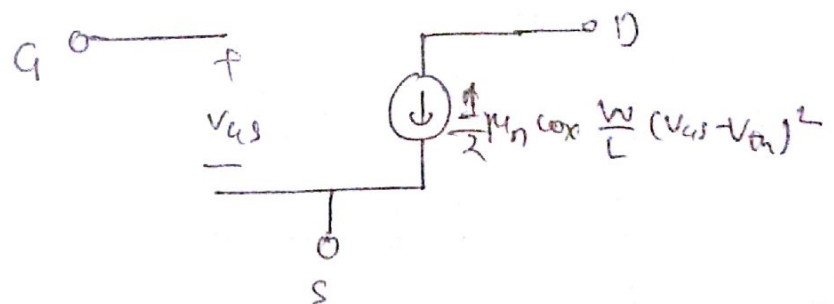

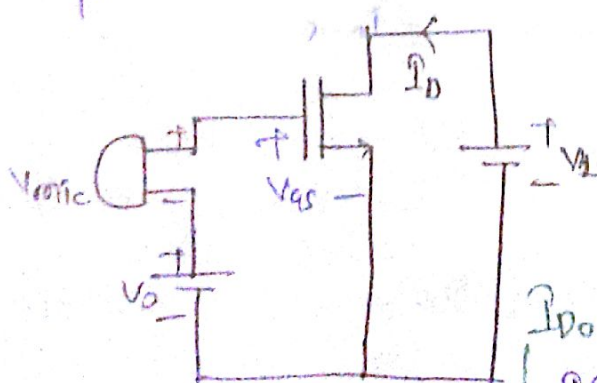* Small signal operation:- In this signal comes in is small in amplitude.



$$V_{gs} = V_0 + V_m \sin \omega t$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_0 + V_m \sin \omega t - V_{th})^2$$

If V_m is small, $V_m \ll V_0 - V_{th}$




$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_0 - V_{th})^2 \left(1 + \frac{V_m \sin \omega t}{V_0 - V_{th}} \right)$$

Assume: $(1+E)^2 = 1+2E$

$$I_D = I_{D0} + 2 \frac{I_{D0}}{V_{GS} - V_{th}} V_m \sin \omega t$$

Signal current

Bias current

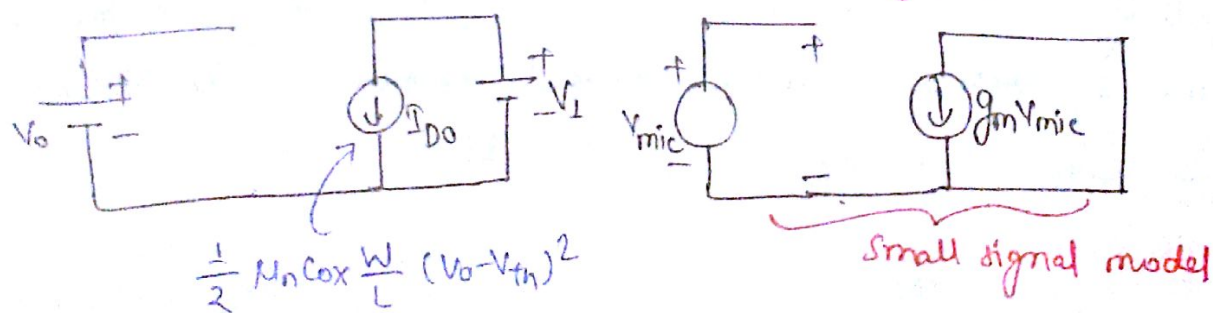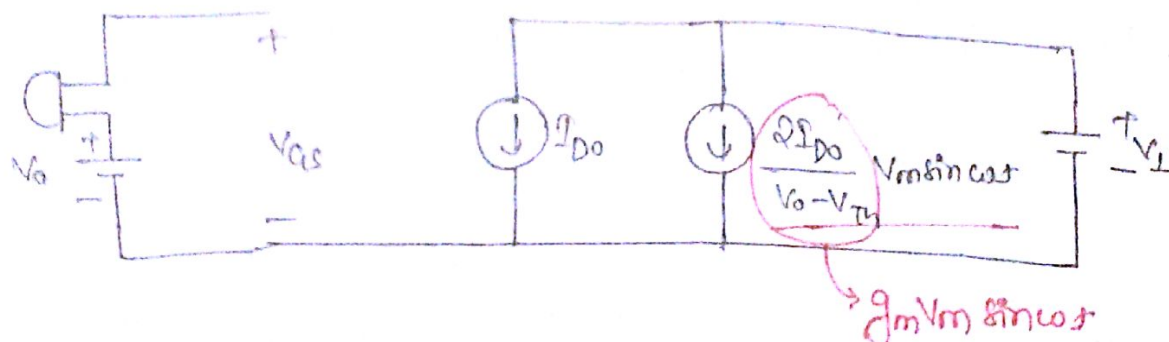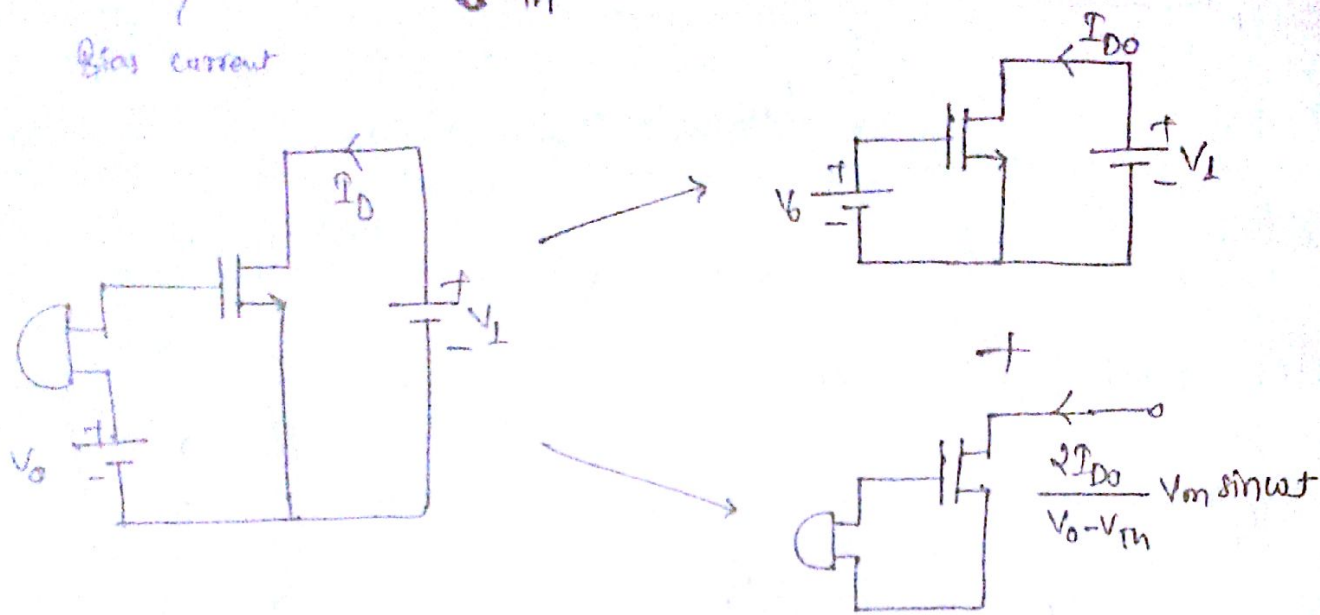

* The small signal consists of something that represents only changes in the currents and voltages.

* Everything which does not change with time, it has zero value in small signal model.