


Lecture - 29

* AC impedances of degenerated CS stage:-


Input impedance:

$$R_{in} = \infty$$


at low frequencies

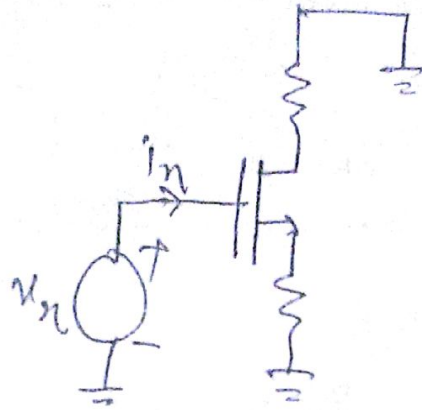



Output impedance: $\lambda > 0$

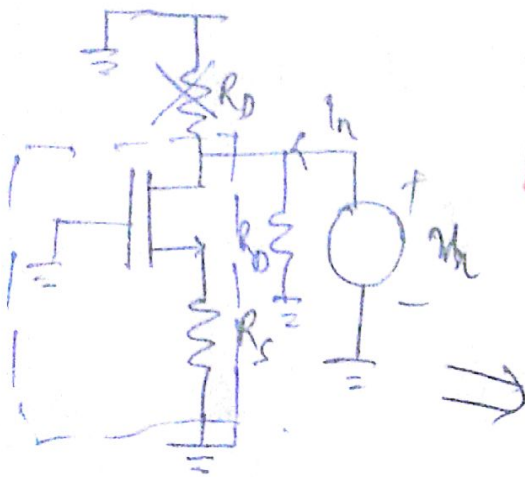
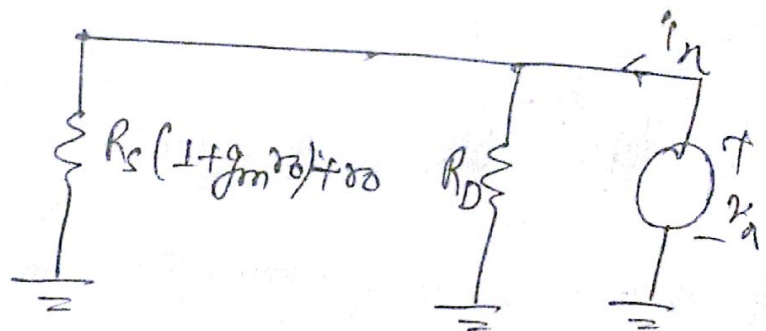
$$R_{out} = R_D \parallel [R_s (1 + g_m r_o) + r_o]$$




* Biasing Techniques:-

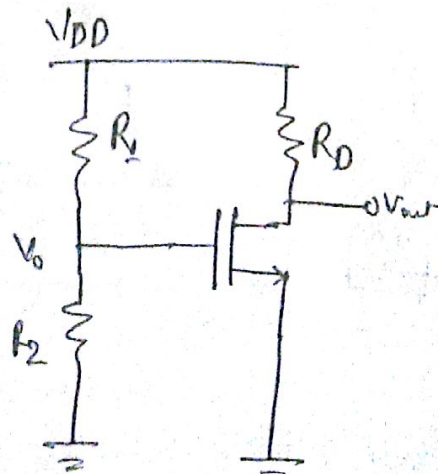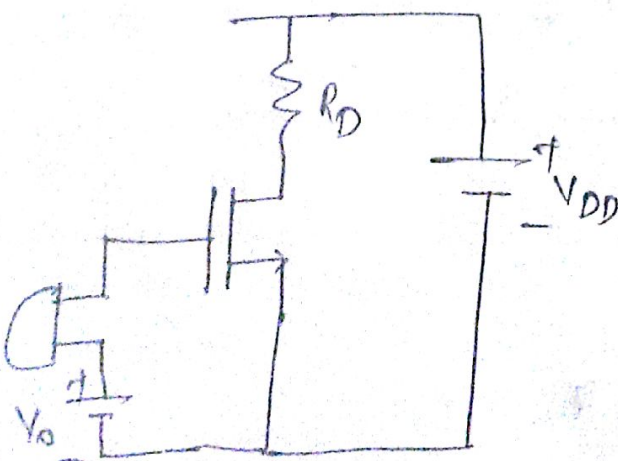

$$V_{DD} \times \frac{R_2}{R_1 + R_2} = V_0$$


Observation:-

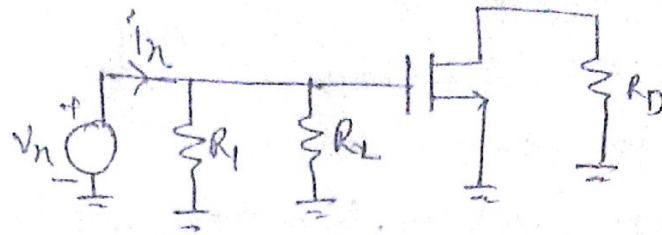- ① Input impedance has fallen to $R_1 \parallel R_2$.



$$R_{in} = R_1 \parallel R_2$$

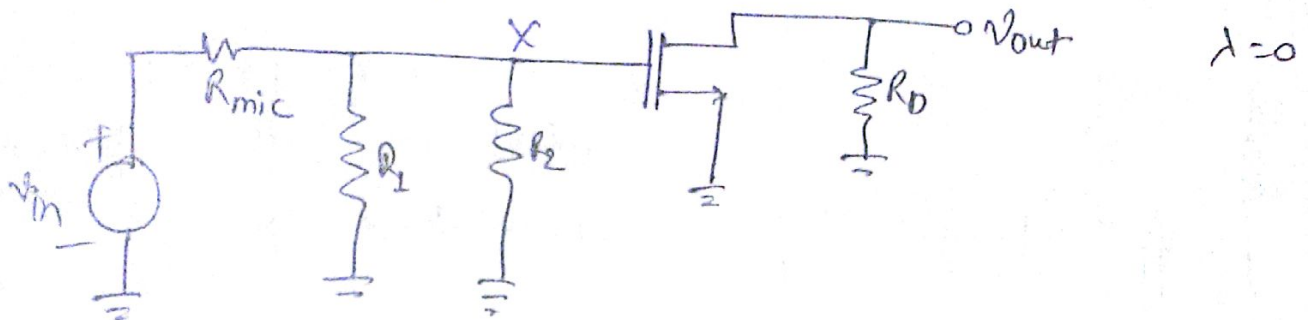connect a microphone which has some internal resistance.




$$\frac{V_{out}}{V_{in}} = \frac{V_{in}}{V_{in}} \times \frac{V_{out}}{V_{in}} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{mic}} \times (-g_m R_D)$$

→ We have an attenuation factor as a result of R_1, R_2 biasing components.

We choose $R_1 \parallel R_2 > R_{mic}$ to minimize the attenuation.

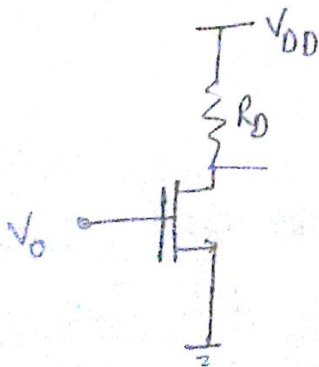- ② Can we increase R_D to increase the gain?





If R_D increases then V_D decreases therefore MOS goes closer to triode region. We can increase R_D only to the point where drain voltage is below the gate by one threshold voltage not more.

$$V_{DD} - I_D R_D \geq V_0 - V_{th}$$

$$\frac{V_{DD} - V_0 + V_{th}}{I_D} \geq R_D$$

③

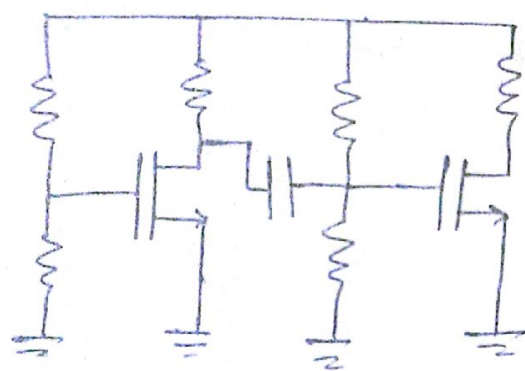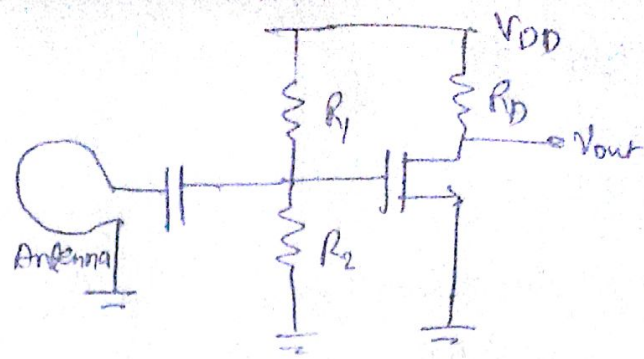→ This tells us that anytime we have an amplifier or any circuit that have some bias conditions and we want to drive it with something (antenna, microphone or another amplifier) we have to worry about this agreement between the bias and conditions that the preceding stage produces.



ok for matching the bias of both devices we place a capacitor between these stages.

④


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)^2$$

sensitive to: V_{DD} , process (μ_n, C_{ox}, V_{TH}), temperature

So generally the circuit is not so stable.

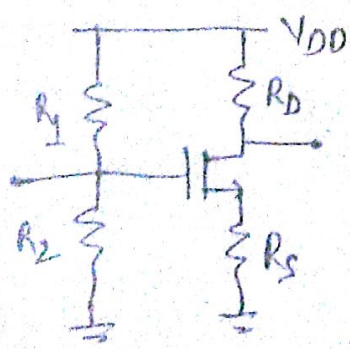⑤ Reduced sensitivity with degenerated CS stage




→ If the gate voltage is perturbed by some amount ΔV due this V_{GS} does not changes by ΔV it changes by less than ΔV and that means I_D is less sensitive to ΔV .

$$V_{DD} \frac{R_2}{R_1 + R_2} = V_{GS} + I_D R_S$$

$$\therefore I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

* Self bias CS stage:-

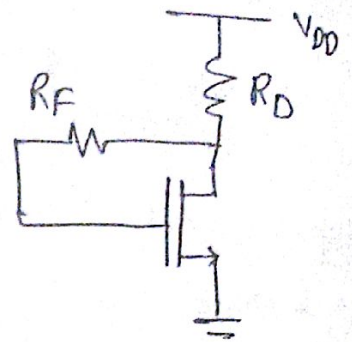* If V_{th} drops then I_D wants to increase, we draw larger current through R_D so drain voltage goes down. Since no current goes through gate so gate voltage is equal to drain voltage therefore V_{GS} voltage goes down. Thus, I_D current goes down. Therefore this circuit is less sensitive to parameters. It has self correction mechanism.




$$\text{Drain voltage} = V_{DD} - I_D R_D = \text{Gate voltage}$$

$$\therefore I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - I_D R_D - V_{th})^2$$

* The device is always in ~~saturation~~ Saturation because the drain does not go below the gate so device is always in saturation.


Example:-

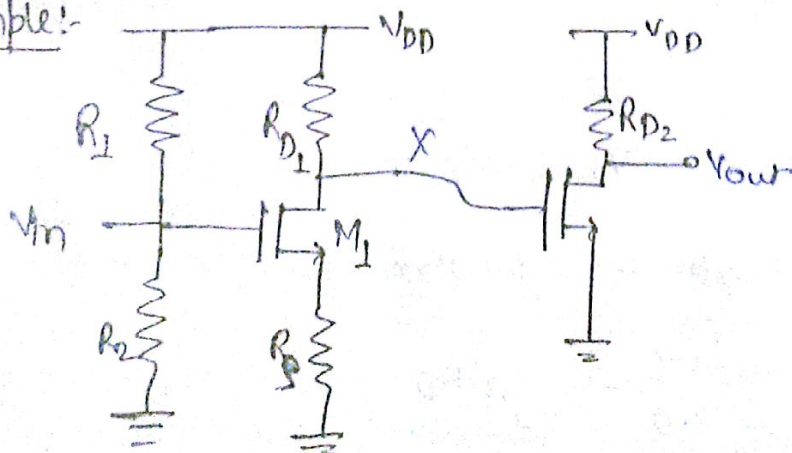

$$\frac{V_{out}}{V_{in}} = \frac{V_X}{V_{in}} \times \frac{V_{out}}{V_X} = - \frac{R_{D1}}{\frac{1}{g_{m1}} + R_S} \cdot (-g_{m2} R_{D2})$$

Ans

Common Gate Topology:-

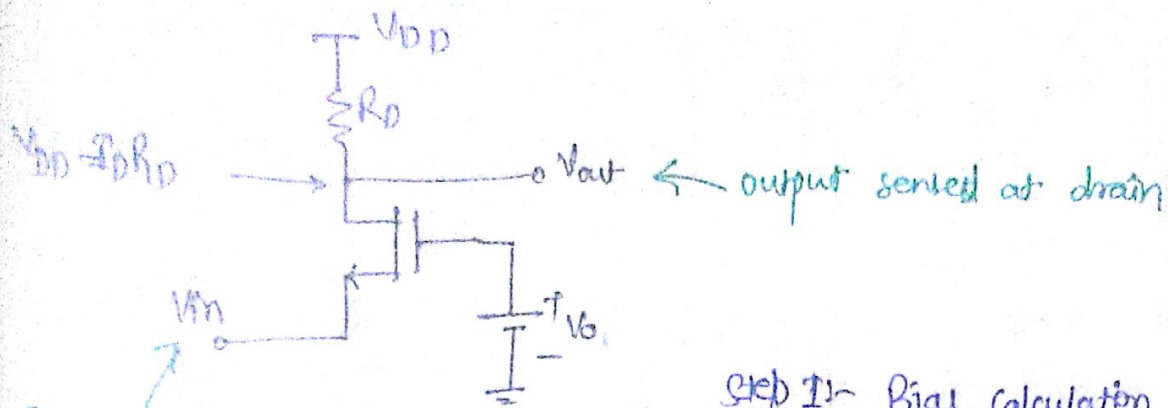

Input applied to ~~source~~ source



Step I:- Bias calculation

Step II:- Small signal analysis

* Suppose source voltage goes up by ΔV and gate voltage is constant so V_{GS} decreases therefore I_D decreases so output goes up by some amount. Therefore this does not invert i.e. it does not have negative sign in gain.

Lecture - 40


Small signal properties:-

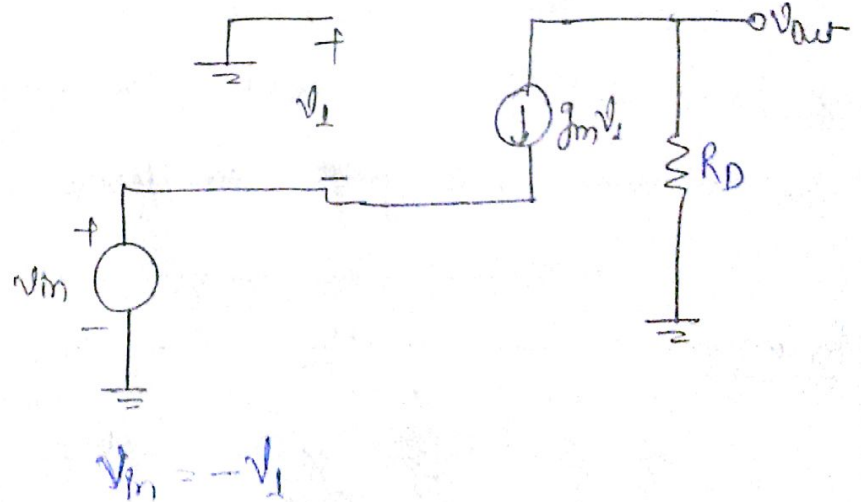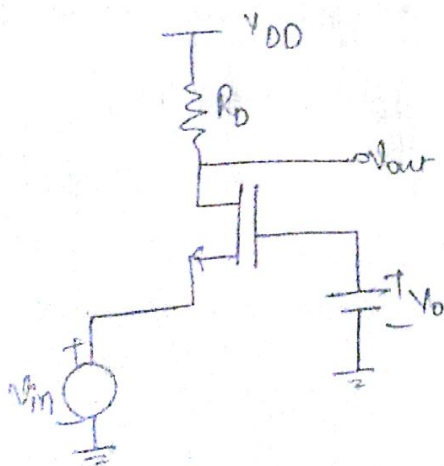

$$V_{out} = -g_m V_{gs} R_D = -g_m (-V_{in}) R_D$$

$$\boxed{\frac{V_{out}}{V_{in}} = g_m R_D}$$

Req


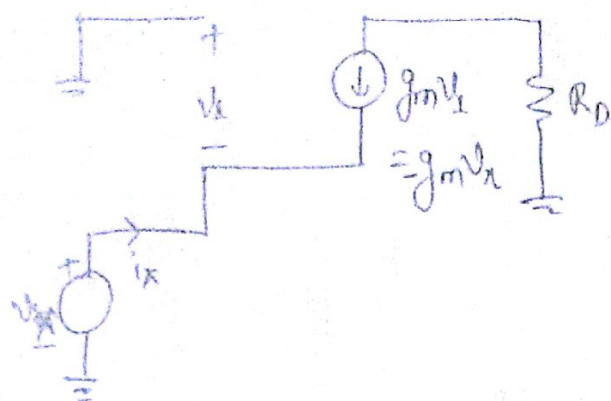


$$i_n = +g_m v_n$$

$$R_{in} = \frac{v_n}{i_n} = \frac{1}{g_m}$$

It's relatively very low.


Applications:-

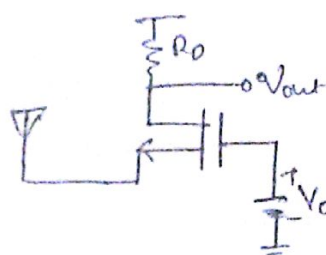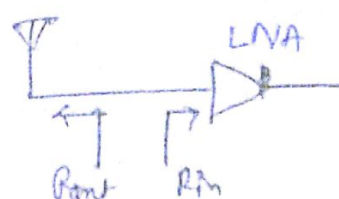

∴ we require input resistance of LNA be equal to the resistance of an antenna.

* The common gate matches impedances.


Rout

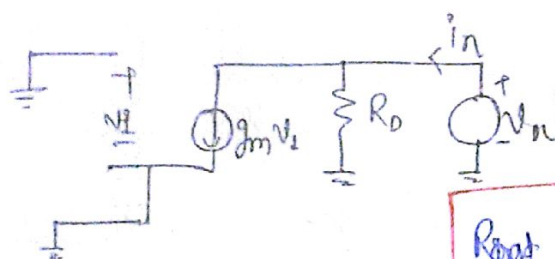

$$v_1 = 0 \Rightarrow g_m v_1 = 0$$



$$R_{out} = \frac{v_n}{i_n} = R_D$$

Example:-

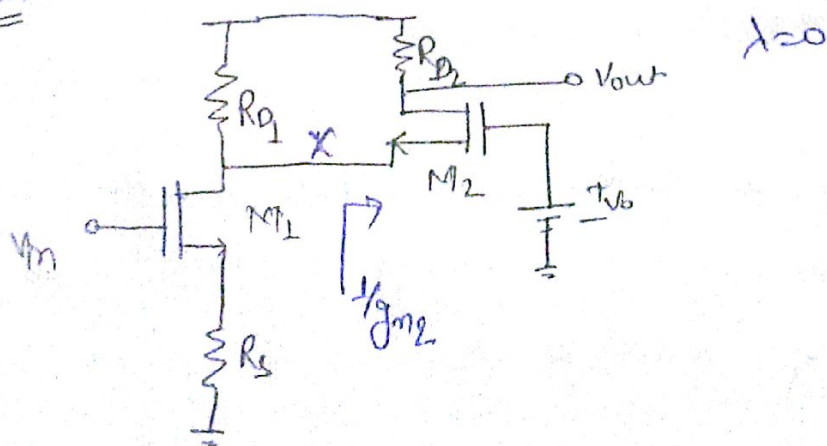

$$\frac{v_{out}}{v_{in}} = \frac{v_n}{v_{in}} \times \frac{v_{out}}{v_n} = \left(- \frac{R_{D2} \parallel \frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S} \right) (g_{m2} R_{D2})$$

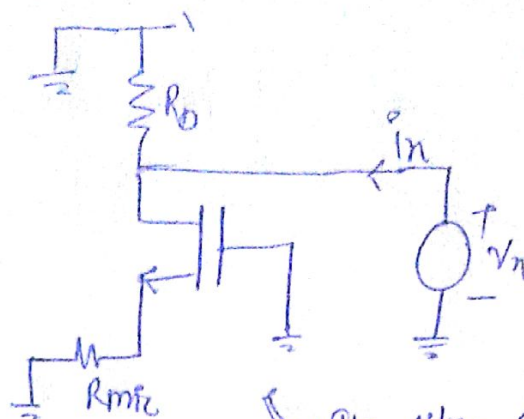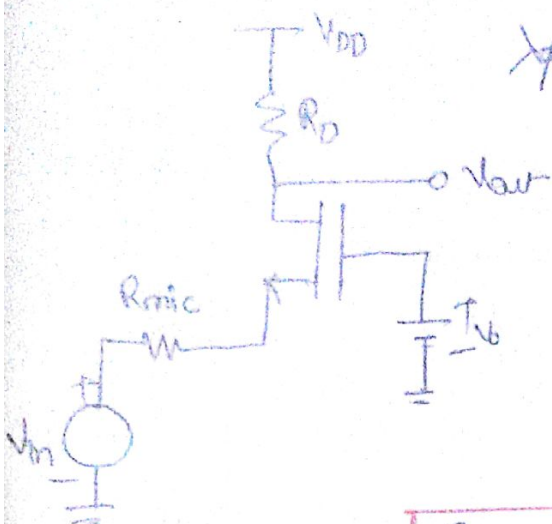Output resistance of CG stage in a special case:-





Its like CE stage with degeneration

$$R_{out} = R_D \parallel [(1 + g_m R_D) R_S + r_o]$$

Bias design:-

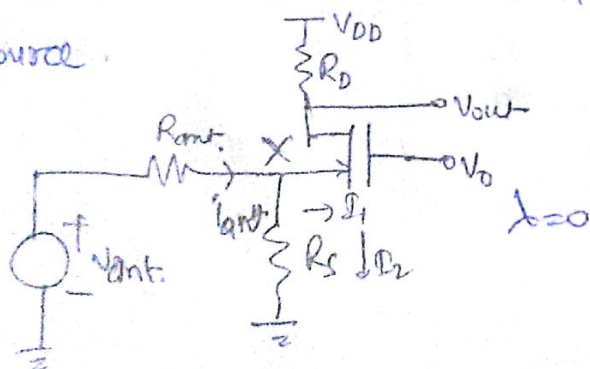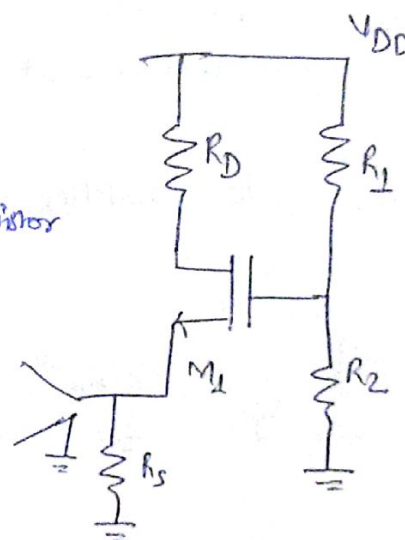- * The antenna does not allow dc.
- * To bias properly, we just connect a resistor \$R_S\$ with antenna.
- * Since the antenna is not an ideal source.



When the current goes to divider then it splits up. When current goes through \$R_S\$ is undesirable. For reducing this current we just increase the value of resistance \$R_S\$.

$$I_1 = \frac{R_S}{R_S + 1/g_m} I_{ant}$$

\$R_S \gg 1/g_m\$ for maximize the current \$I_1\$.

$$\frac{V_{out}}{V_{in}} = \frac{V_n}{V_{in}} \times \frac{V_{out}}{V_n} = \left(\frac{R_s}{R_s + R_{out}} \right) \left(\frac{g_m R_D}{1 + g_m R_D} \right)$$

$$= \left(\frac{\left(\frac{1}{g_m} \parallel R_s \right)}{\left(\frac{1}{g_m} \parallel R_s \right) + R_{out}} \right) \cdot (g_m R_D)$$

Example

$$V_{DD} = 1.5V, P = 1.5mW, \mu_n C_{ox} = 100 \mu A/V^2, V_{TH} = 0.5V, \lambda = 0$$

$$\frac{W}{L} = 50$$

$$\text{Total current} = 1mA$$

$$\text{Assume } I_D \approx 1mA$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\frac{2 \times 10^{-3}}{100 \times 10^{-9} \times 50} = (V_{GS} - V_{TH})^2$$

$$\Rightarrow V_{GS} = 0.63V + V_{TH} = 1.13V$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2 \times 10^{-3}}{0.13} = 3.2ms = \frac{1}{316 \Omega}$$

$$R_s = \frac{10}{g_m} = 3.16K\Omega$$

we can't do that because if 1mA flows through it then voltage across it will be 3.16V which is not appropriate.


$$R_{s,max} = \frac{V_{DD} - 0.63}{1mA} = 370\Omega$$

$$I_D R_D \leq V_{TH} \quad (\text{for } M_1 \text{ be in saturation})$$

$$R_D \leq \frac{V_{TH}}{I_D}$$

$$R_D = 500\Omega$$
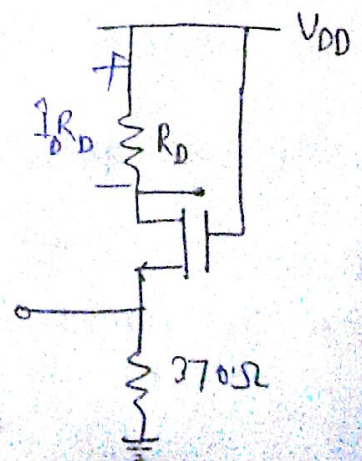
$$A_v = \underline{\underline{g_m R_D = 1.6}}$$



If we double $\frac{W}{L}$ for increasing gain,

$$\frac{W}{L} = 100$$

device becomes slower larger width and capacitance.

$$V_{GS} = 0.947V$$

$$R_S = \frac{V_{DD} - V_{GS}}{I_D} = 550 \Omega$$


$$g_m = \frac{2I_D}{V_{GS} - V_{th}} = 4.5 \text{ mS} = \frac{1}{220 \Omega}$$

So current see 220Ω into the transistor so it flows through the transistor in large values.


$$\underline{g_m R_D = 2.3}$$

Lecture - 41

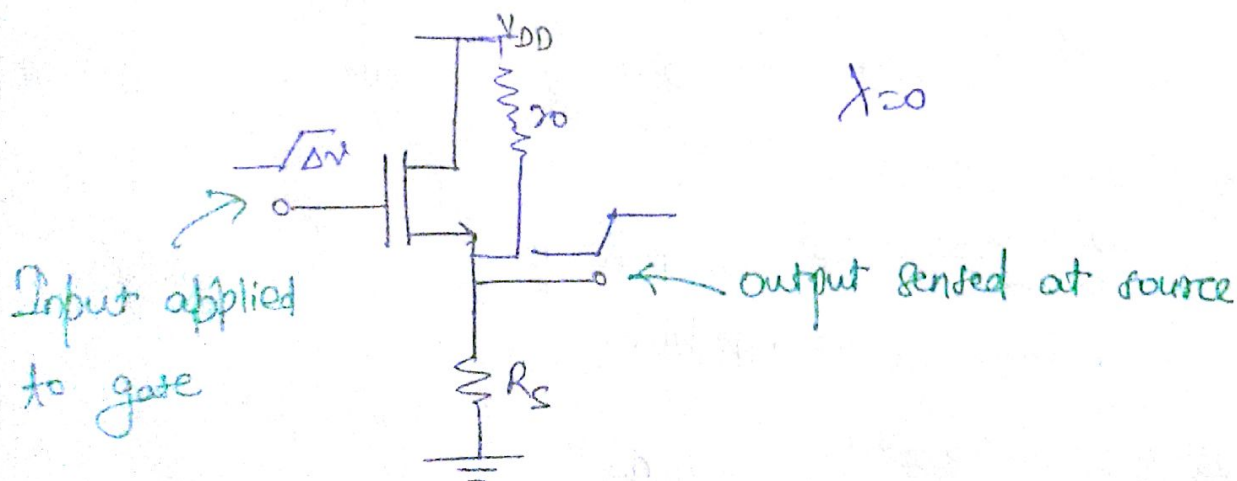* Source Follower Topology - (common drain)



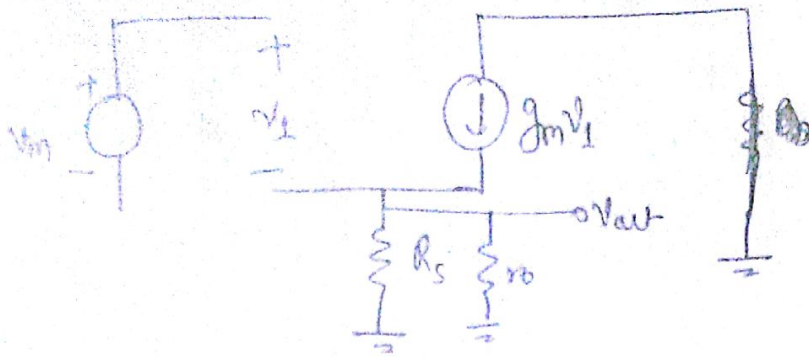* If we apply a change in voltage Δv at input. V_{out} must also go up by some amount because if V_{GS} increases and V_S constant then I_D current increasing but drain current flows through R_S so it also goes up.



$$V_{in} = V_1 + V_{out}$$

$$\Rightarrow V_1 = V_{in} - V_{out}$$

$$g_m (V_{in} - V_{out}) = \frac{V_{out}}{R_S}$$

$$g_m V_{in} = V_{out} \left(\frac{1}{R_S} + g_m \right)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{g_m R_S}{1 + g_m R_S} < 1$$

$$A_v = \frac{\text{resistance b/w source and } \cancel{\text{source}} \text{ ground}}{\frac{1}{g_m} + \text{resistance b/w source and ground}}$$

• Alternative Analysis:-

Theremin equivalent $\rightarrow$

$$V_{in} = V_{Th}$$



because $g_m V_1 \gg 0 \Rightarrow V_1 \gg 0$


$$V_n = -V_1$$

$$\Rightarrow -g_m V_n + I_n = 0$$

$$\Rightarrow \frac{V_n}{I_n} = \frac{1}{g_m} = R_{Th}$$

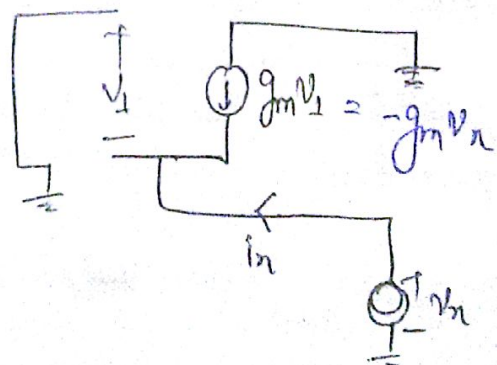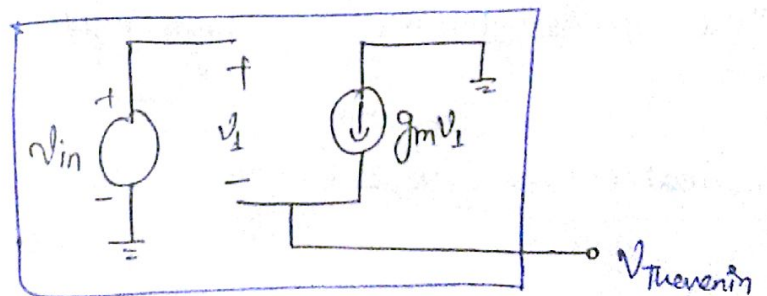$\leftarrow$ like a diode connected device.



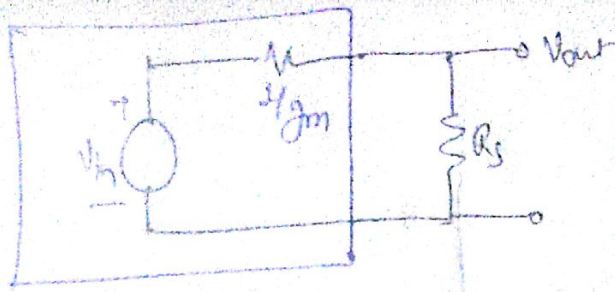

This gives same result as previous approach.


If $\lambda \neq 0$ then

$$A_v = \frac{R_s \parallel r_o}{R_s \parallel r_o + 1/g_m}$$

R_{in} :

$R_{in} = \infty$ At low frequency

R_{out} :

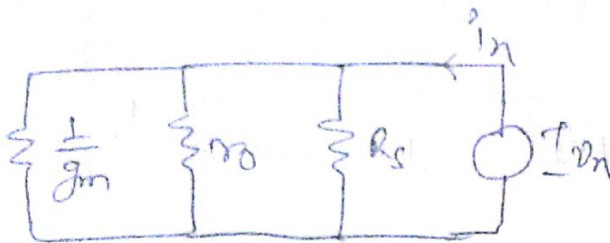


$$R_{out} = \frac{V_n}{i_n} = \left(\frac{1}{g_m} \parallel r_o \parallel R_s \right)$$

* The source follower has high input impedance and low output impedance.

Application of source follower:-

* If we connect an antenna of 50Ω the R_o becomes is in parallel with 50Ω so A_v reduces


$\lambda = 0$

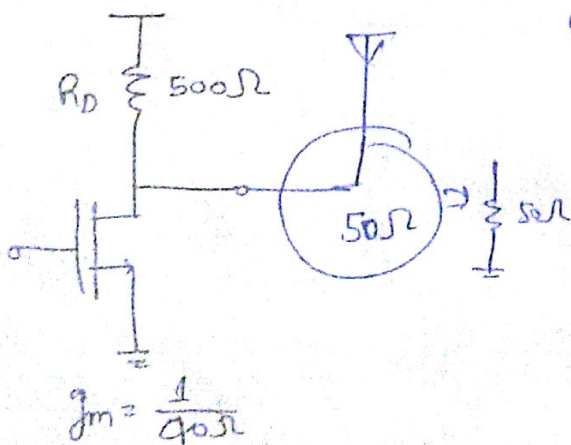

$$A_v = -\frac{1}{40\Omega} (500 \parallel 50) = -1.14$$

* We place a buffer to keep the gain of this device intact.


$$A_v = -g_m R_D = -12.5$$

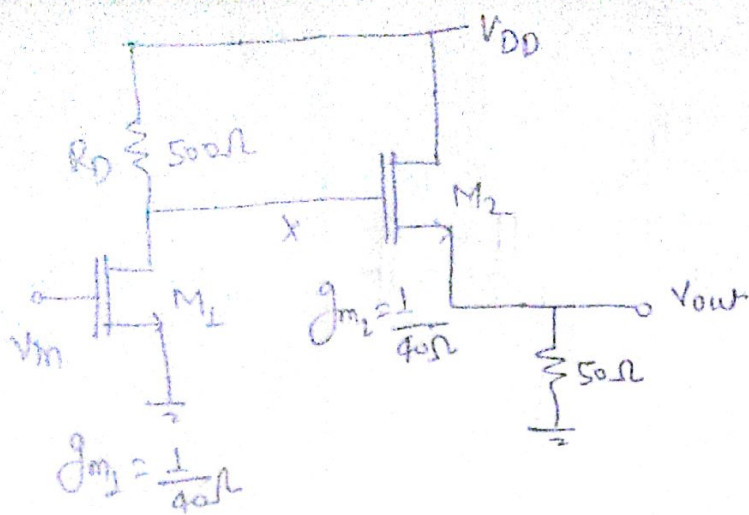

$$\frac{V_{out}}{V_{in}} = \frac{V_n}{V_{in}} \times \frac{V_{out}}{V_n} = (-12.5) \left(\frac{50}{50+40} \right) = -6.9$$

which is better than without buffer.


Example:

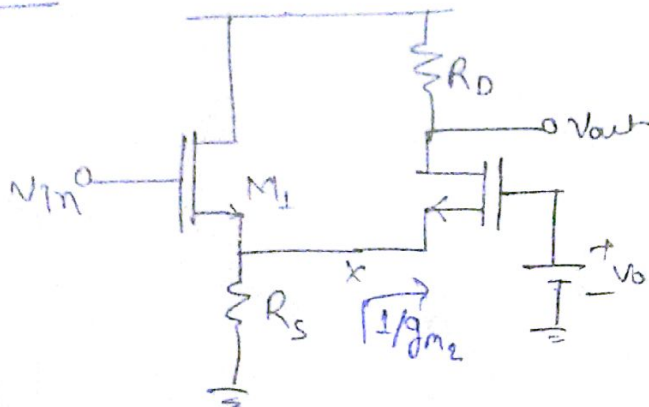


$$\frac{V_{out}}{V_{in}} = \frac{V_n}{V_{in}} \times \frac{V_{out}}{V_n} = \left[\frac{(R_S \parallel 1/g_{m2})}{(R_S \parallel 1/g_{m2}) + (1/g_{m2})} \right] \times [g_{m2} R_D]$$

* Bias design:-

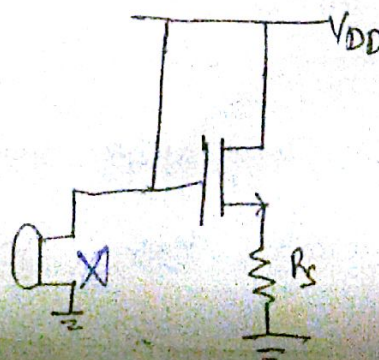→ we cannot apply signal to the device because it is connected to the short ckt.




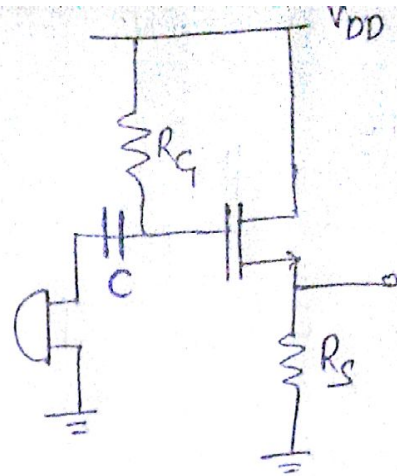→ In some cases, the input device imposes its own dc value (like s.c), to avoid this we just connect a capacitor between them.



Summary:-


CS

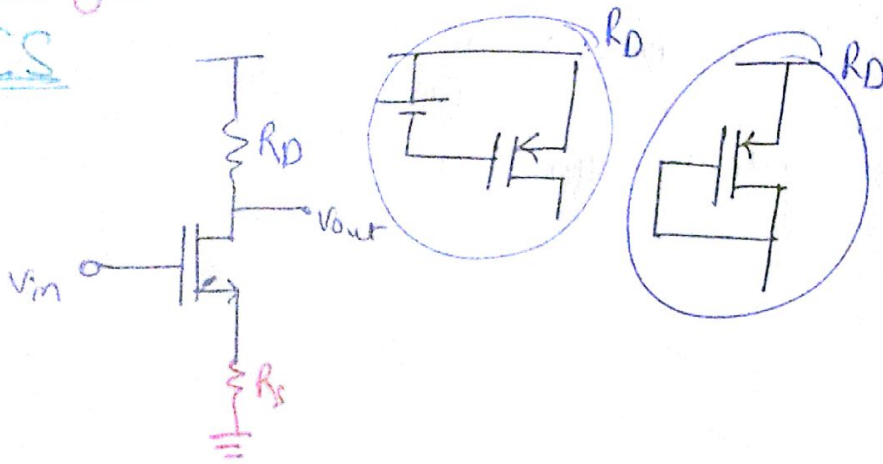

20


$$A_v = - \frac{R_D}{R_S + 1/g_m}$$

CG

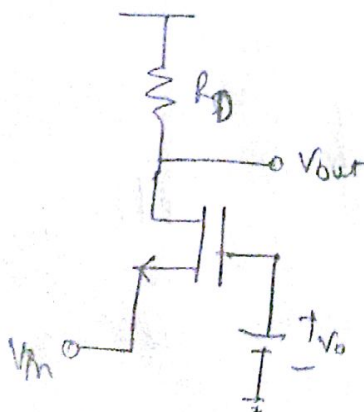

$$A_v = +g_m R_D$$

SF

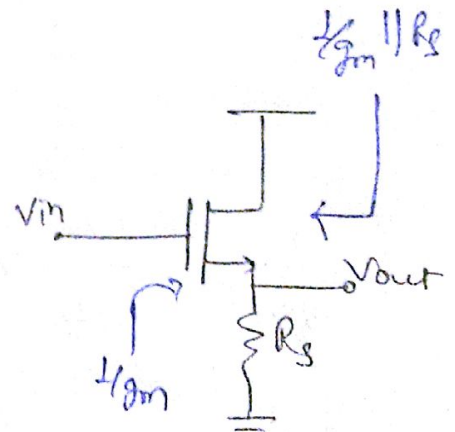

$$A_v = \frac{R_S}{R_S + 1/g_m}$$

Because of its low output impedances (antenna, mic. etc) That's why we have use source followers as a buffer.