

TUTORIAL SHEET - 2

(DIGITAL CIRCUITS AND SYSTEMS)

1. (a)

$$\textcircled{1.} \quad F(A, B, C, D) = \pi(1, 5, 12, 15)$$

$$F(A, B, C, D) = \sum(0, 2, 3, 4, 6, 7, 8, 9, 10, 11, 13)$$

(a)

$$F(A, B, C, D) = I_0 \bar{B} \bar{C} \bar{D} + I_1 \bar{B} \bar{C} D + I_2 \bar{B} C \bar{D} + I_3 \bar{B} C D + I_4 B \bar{C} \bar{D} + \dots + I_{15} B C D$$

	I_0 000 $\bar{B} \bar{C} \bar{D}$	I_1 001 $\bar{B} \bar{C} D$	I_2 010 $\bar{B} C \bar{D}$	I_3 011 $\bar{B} C D$	I_4 100 $B \bar{C} \bar{D}$	I_5 101 $B \bar{C} D$	I_6 110 $B C \bar{D}$	I_7 111 $B C D$
$A=0 \quad \bar{A}$	$\textcircled{0}$	1	$\textcircled{2}$	$\textcircled{3}$	$\textcircled{4}$	5	$\textcircled{6}$	$\textcircled{7}$
$A=1 \quad A$	$\textcircled{8}$	$\textcircled{9}$	$\textcircled{10}$	$\textcircled{11}$	12	$\textcircled{13}$	$\textcircled{14}$	15
	1	A	1	1	$\bar{A}$	A	1	$\bar{A}$

1. (b)

(b) 2 Variable for select lines $\leftarrow$
2 for inputs

B & C $\rightarrow$ select lines

A & D $\rightarrow$ input lines

	I_0 00 $\overline{B}\overline{C}$	I_1 01 $\overline{B}C$	I_2 10 $B\overline{C}$	I_3 11 BC
$\overline{A}\overline{D}$	0	2	4	6
$\overline{A}D$	1	3	5	7
$A\overline{D}$	8	10	12	14
AD	9	11	13	15
	$A+\overline{D}$	1	$\overline{D}$	$\overline{A}$

$$\overline{A}\overline{D} + \overline{A}D + AD = A + \overline{D}$$

$$\overline{A}\overline{D} + A\overline{D} = \overline{D}$$

$$\overline{A}\overline{D} + \overline{A}D = \overline{A}$$


2.

(2.)

$$F(W, X, Y, Z) = \sum m(3, 4, 5, 7, 10, 14) + \sum d(1, 6, 15)$$

	I_0 $\bar{Y}\bar{Z}$	I_1 $\bar{Y}Z$	I_2 $Y\bar{Z}$	I_3 YZ
$\bar{W}\bar{X}$	0	(1)	2	(3)
$\bar{W}X$	(4)	(5)	(6)	(7)
$W\bar{X}$	8	9	(10)	11
WX	12	13	(14)	(15)
	$\bar{W}X$	$\bar{W}$ or $\bar{W}X$	$W+X$ or W	$\bar{W}+X$ or $\bar{W}$

→ considering don't care.

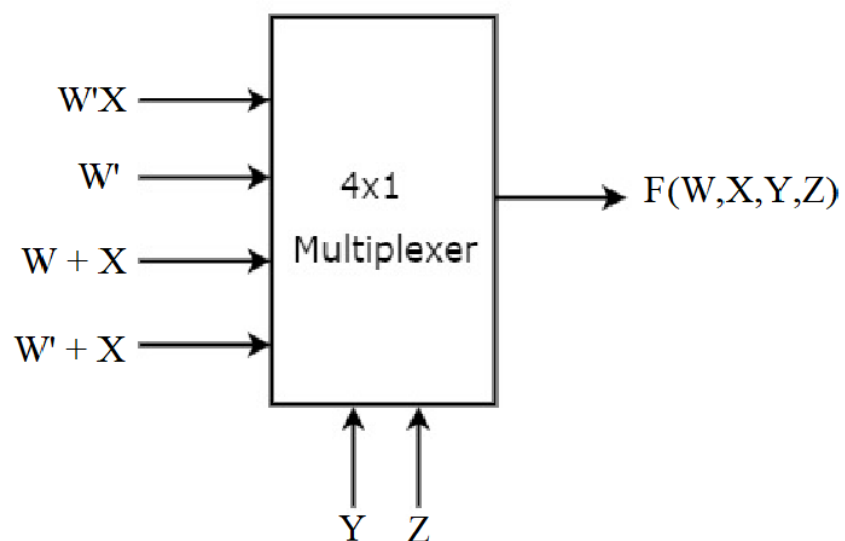

4.

Truth Table :

BCD Inputs				excess-3 Outputs			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


$$W = \sum m(5, 6, 7, 8, 9)$$

$$X = \sum m(1, 2, 3, 4, 9)$$

$$Y = \sum m(0, 3, 4, 7, 8)$$


$$Z = \sum m(0, 2, 4, 6, 8)$$

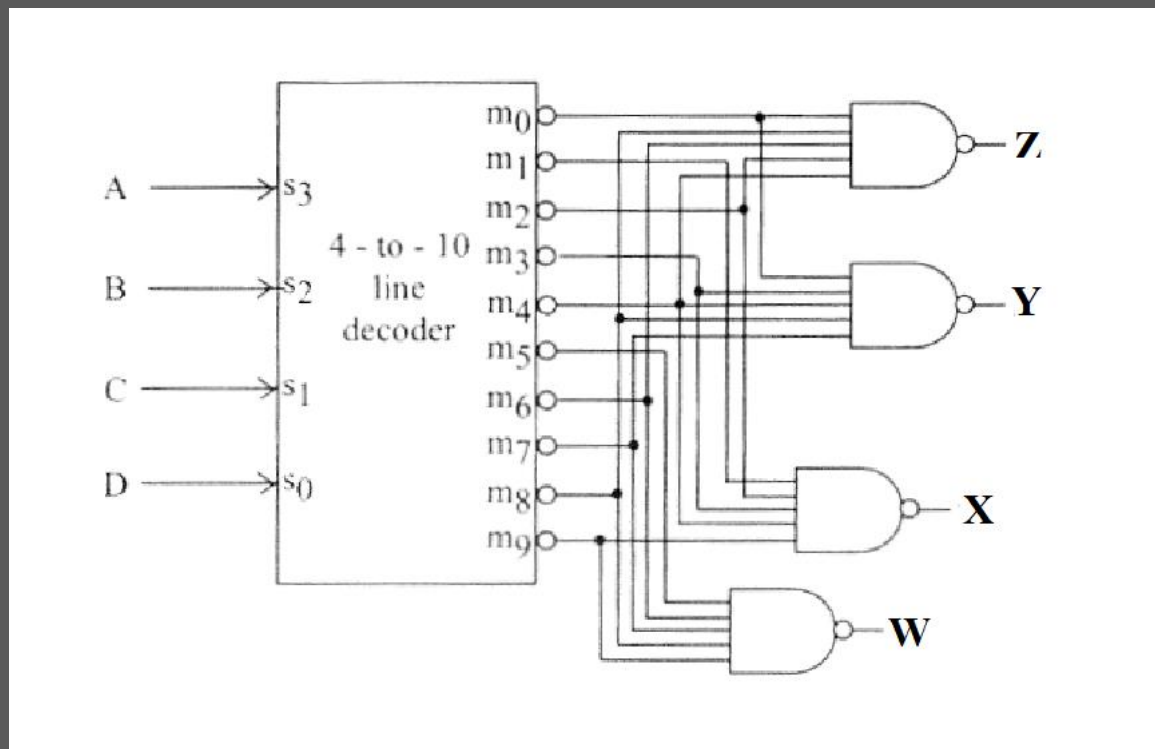- Since decoder output are active low, NAND gates are required.
- So four 5-input NAND gates are needed with corresponding to the min-terms of the excess-3 output.



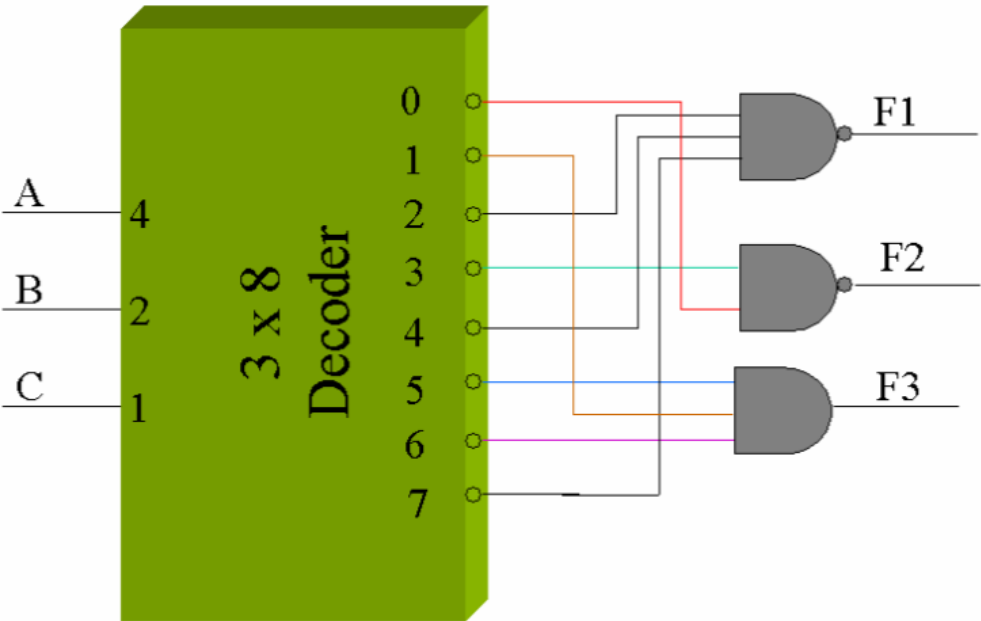3.

Minimize the number of inputs in the external gates.



5.

Truth Table of DEMUX :

Data Input	Select Inputs			Outputs							
D	S ₂	S ₁	S ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
D	0	0	0	0	0	0	0	0	0	0	D
D	0	0	1	0	0	0	0	0	0	D	0
D	0	1	0	0	0	0	0	0	D	0	0
D	0	1	1	0	0	0	0	D	0	0	0
D	1	0	0	0	0	0	D	0	0	0	0
D	1	0	1	0	0	D	0	0	0	0	0
D	1	1	0	0	D	0	0	0	0	0	0
D	1	1	1	D	0	0	0	0	0	0	0

Truth Table of decoder :

Inputs			Outputs			
EN	A	B	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

